

Analog Dialogue

StudentZone—Activity: BJT Current Mirror

Doug Mercer, Consulting Fellow

and Antoniu Miclaus, System Applications Engineer

Objective:

The goal of this activity is to study the bipolar junction transistor (BJT) current source or current mirror. Important attributes for current sources include high output resistance with a wide range of voltage compliance and rejection of external variations such as power supply or temperature.

Background

A current mirror is a circuit block that functions to produce a copy of the current flowing into or out of an input terminal by replicating the current in an output terminal. The simple two-transistor implementation of the current mirror is based on the fundamental relationship that two equal size transistors at the same temperature with the same V_{BE} have the same drain or collector current. An important feature of the current mirror is a relatively high output resistance that helps keep the output current constant regardless of load conditions. Another feature of the current mirror is a relatively low input resistance that helps to keep the input current constant regardless of drive conditions. The current being copied can be, and often is, a varying signal current. The current mirror is often used to provide bias currents and active loads in amplifier stages.

Materials:

- ADALM2000 active learning module
- Solderless breadboard
- Jumper wires
- Two 1 kΩ resistors (values matched as closely as possible, or measured to three digits or better)
- Two small signal NPN transistors (2N3904 or SSM2212)
- One dual op amp (such as ADTL082)
- Two 4.7 µF decoupling capacitors

Directions

A good way to measure the characteristics of the current mirror is to reuse the same basic configuration that was used in the common-emitter BJT curve tracer experiments. The input and output resistors R1 and R2 are now both 1 k Ω . Be sure to accurately measure (with the most significant figures possible) the actual values of R1 and R2. This is to ensure accurate measurement of the input and output current of the mirror. $I_{\rm IN}$ will be equal to the AWG2 output voltage at W1 divided by the value of R1. $I_{\rm OUT}$ will be the voltage measured by Scope Channel 2 divided by the value of R2. Diode connected transistor Q1 is connected across the base and emitter terminals of Q2.

In the current mirror configuration, the op amp serves as a virtual ground at the mirror input (base) node to convert the voltage steps from AWG2 (W2) into current steps through the $1 k\Omega$ resistor.



Figure 1. Current mirror test circuit.

If you don't want to use the op amp configuration, the simplified configuration shown in Figure 2 can be used as well.



Figure 2. Alternate, simple current mirror test circuit.





Figure 3. Breadboard connection of current mirror test circuit (with op amp).



Figure 4. Breadboard connection of simple current mirror test circuit.

Hardware Setup

Load the stairstep.csv file for the W2 channel of the signal generator, and set the amplitude to 3 V p-p with the offset set to 1.5 V. V_{cc} of output device Q2 is measured differentially by scope inputs 1+ and 1-. The mirror output current is measured by scope inputs 2+ and 2- across 1 k Ω resistor R2. The collector voltage is swept using a triangle waveform from AWG 1 (output W1) with 40 Hz frequency. If you are using the op amp setup, make sure that the device is properly connected to the power supplies Vp (5 V) and Vn (-5 V).

Procedure

Configure the oscilloscope instrument to capture several periods of the input signal and the output signal. If you are using the op amp configuration, make sure that the power supplies are turned on.

Plot the two waveforms using the oscilloscope provided by the Scopy tool or via LTspice[®] simulation. Examples are provided in the following figures.



Figure 5. Current mirror waveforms, W2 at 10 kHz frequency, as shown in a Scopy plot.

Now change the frequency of W1 at 200 Hz and plot the two waveforms. An example using an LTspice simulation of the same circuit is provided in Figure 6.



Figure 6. Current mirror waveforms, W1 at 200 Hz, W2 at 40 Hz, as shown in an LTspice plot.

Current Mirror with Base Current Compensation

Modify the simple mirror circuit by adding the base current compensation transistor Q3 as shown in Figure 7. The simple wire connecting the collector of Q1 to its base is replaced by an emitter follower buffer. This improvement to the simple current mirror is referred to as an emitter follower augmented mirror. The current gain of the emitter follower buffer stage (Q2) greatly reduces the gain error caused by the finite base currents of Q1 and Q2.



Figure 7. Current mirror with base current compensation.

Hardware Setup

Load the stairstep.csv file for the W2 channel of the signal generator and set the amplitude to 3 V p-p with the offset set to 1.5 V. V_{CE} of output device Q2 is measured differentially by scope inputs 1+ and 1-. The mirror output current is measured by scope inputs 2+ and 2- across 1 kΩ resistor R2. The collector voltage is swept using a triangle waveform from AWG1 (output W1) with 40 Hz frequency. Connect the positive power supply Vp (+5 V) to the collector of the Q3 transistor.

Procedure

Configure the oscilloscope instrument to capture several periods of the input signal and the output signal. Turn on the positive power supply.

Plot the two waveforms using the oscilloscope provided by the Scopy tool or via LTspice simulation. An example is provided in Figure 9.



Figure 9. Current mirror waveforms, W2 at 10 kHz frequency, as shown in a Scopy plot.



Figure 8. Breadboard connection of a current mirror with base current compensation.

Wilson Current Mirror

A Wilson current mirror or Wilson current source, named after George Wilson, is an improved mirror circuit configuration designed to provide a more constant current source or sink. It provides a much more accurate input to output current gain. Modify the simple mirror into a Wilson current mirror, as shown in Figure 10.



Figure 10. Wilson current mirror.

Hardware Setup

Load the stairstep.csv file for the W2 channel of the signal generator, set the amplitude to 3 V p-p with the offset set to 1.5 V. V_{CE} of output device Q2 is measured differentially by scope inputs 1+ and 1-. The mirror output current is measured by scope inputs 2+ and 2- across 1 kD resistor R2. The collector voltage is swept using a triangle waveform from AWG1 (output W1) with 40 Hz frequency.

Procedure

Configure the oscilloscope instrument to capture several periods of the input signal and the output signal.

Plot the two waveforms using the oscilloscope provided by the Scopy tool or via LTspice simulation. A Scopy plot example is provided in Figure 12.



Figure 12. Wilson current mirror waveforms, W2 at 10 kHz frequency, Scopy plot.



Figure 11. Breadboard connection of Wilson current mirror.

Widlar Current Mirror

Modify the simple mirror into a Widlar Mirror as shown in Figure 13. A Widlar current source is a modification of the basic two-transistor current mirror that incorporates an emitter degeneration resistor for only the output transistor, enabling the current source to generate low currents using only moderate resistor values. The Widlar circuit may be used with bipolar transistors or MOS transistors.



Figure 13. Widlar current mirror.

Hardware Setup

Load the stairstep.csv file for the W2 channel of the signal generator, set amplitude to 3 V peak-to-peak with the offset to 1.5 V. V_{CE} of output device Q2 is measured differentially by scope inputs 1+ and 1-. The mirror output current is measured by scope inputs 2+ and 2- across 1 k Ω resistor, R2. The collector voltage is swept using a triangle waveform from AWG1 (output W1) with 40 Hz frequency.

Procedure

Configure the oscilloscope instrument to capture several periods of the input signal and the output signal.

Plot the two waveforms using the oscilloscope provided by the Scopy tool or via LTspice simulation. A Scopy plot example is provided in Figure 15.



Figure 15. Widlar current mirror waveforms, W2 at 10 kHz frequency, Scopy plot.

Questions:

- Can you name one advantage and one disadvantage of the current mirror circuit with base current compensation?
- Can you name one advantage and one disadvantage of the Wilson current mirror?



Figure 14. Breadboard connection of Widlar current mirror.



About the Author

Doug Mercer received his B.S.E.E. degree from Rensselaer Polytechnic Institute (RPI) in 1977. Since joining Analog Devices in 1977, he has contributed directly or indirectly to more than 30 data converter products and he holds 13 patents. He was appointed to the position of ADI Fellow in 1995. In 2009, he transitioned from full-time work and has continued consulting at ADI as a Fellow Emeritus contributing to the Active Learning Program. In 2016 he was named Engineer in Residence within the ECSE department at RPI. He can be reached at doug.mercer@analog.com.



About the Author

Antoniu Miclaus is a system applications engineer at Analog Devices, where he works on ADI academic programs, as well as embedded software for Circuits from the Lab[®], QA automation, and process management. He started working at Analog Devices in February 2017 in Cluj-Napoca, Romania. He is currently an M.Sc. student in the software engineering master's program at Babes-Bolyai University and he has a B.Eng. in electronics and telecommunications from Technical University of Cluj-Napoca. He can be reached at antoniu.miclaus@analog.com.



For regional headquarters, sales, and distributors or to contact customer service and technical support, visit analog.com/contact.