

StudentZone— ADALM2000 Activity: Generating Sine Waves from Triangle Waves

Doug Mercer, Consulting Fellow and
Antoniu Miclaus, System Applications Engineer

Objective

The circuit we are evaluating in this activity generates an approximate sine wave from a triangle wave by using the properties of the differential pair of transistors contained in the SSM2212 NPN matched transistor pair. We know that the transconductance of a differential pair of transistors is defined as:

$$g_m = I_o \tanh \frac{V_{IN}}{2V_T} \quad (1)$$

Where I_o is the differential pair tail current, V_{IN} is the differential input voltage, and V_T is the thermal voltage, which is about 26 mV at room temperature.

Materials

- ▶ [ADALM2000](#) Active Learning Module
- ▶ Solderless breadboard
- ▶ Jumper wires
- ▶ One 10 kΩ resistor
- ▶ Four 4.7 kΩ resistors
- ▶ One 2.2 kΩ resistor
- ▶ Two 220 Ω resistors
- ▶ One 390 Ω resistor
- ▶ One 500 Ω potentiometer
- ▶ One 100 pF capacitor
- ▶ Two small signal NPN transistors (SSM2212 NPN matched pair)
- ▶ One operational amplifier (OP27)

Description

Construct the circuit in Figure 1 on your solderless breadboard. The +5 V (Pin 7) and -5 V (Pin 4) power supply connections for the OP27 amplifier are not pictured in the schematic, but remember to connect them or the circuit will not function.

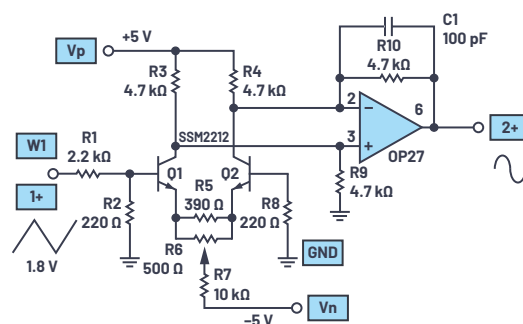


Figure 1. Differential pair triangle to sine converter.

Set the W1 to the following:

- ▶ Amplitude (peak-to-peak) = 3.6 V
- ▶ Offset = 0 V
- ▶ Frequency = 1 kHz
- ▶ Triangle wave

Adjust the 500 Ω potentiometer, R6, for the best symmetry in the output sine wave shape. Using the FFT display and looking for the minimum even order distortion may be a good way to test the quality of the output sine wave. You may want to adjust the amplitude and DC offset of the input triangle wave to see if that can improve the odd order harmonics in the output.

In the case of this circuit, the output voltage will be approximately:

$$V_o = \frac{R_L I_o \tanh \frac{V_{IN}}{2V_T}}{2} \quad (2)$$

Where R_L represents the 4.7 kΩ load resistors on the output. The division by 2 happens because we only take a single-ended output, not a differential output.

So, the output voltage will be a function of the input voltage and the hyperbolic tangent. The first few terms of the Taylor series of the sine and hyperbolic tangent functions are as follows in Equation 3 and Equation 4.

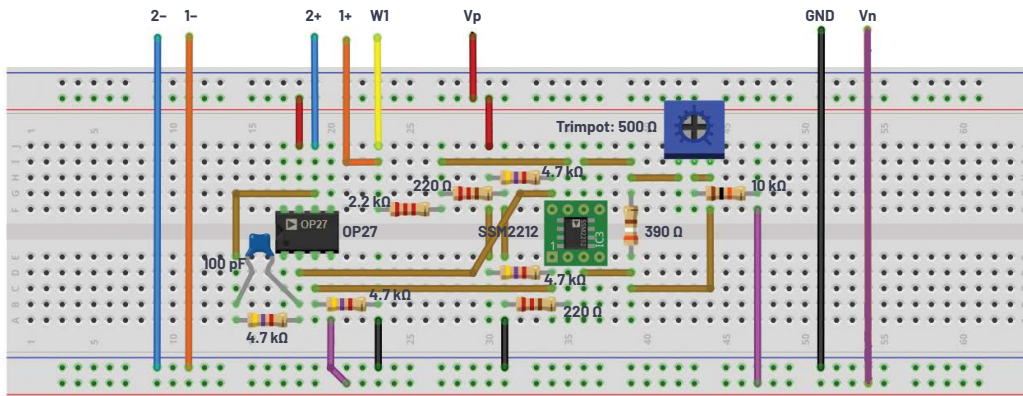


Figure 2. Differential pair triangle to sine converter breadboard connections.

Sine:

$$x - \frac{x^3}{3!} + \frac{x^5}{5!} \quad (3)$$

Hyperbolic tangent:

$$x - \frac{x^3}{3} + \frac{2x^5}{15} \quad (4)$$

Comparing the two Taylor series will show that they both have first-order linearity. What this means is that if we apply a triangle wave to a differential pair with a hyperbolic tangent transfer function and keep the amplitude low—that is, on the order of $2V_T$ —the output should be nearly indistinguishable from a sine wave. The purpose of the 2.2 kΩ and 220 Ω resistors at the input of the differential pair (base of Q1) is to attenuate the triangle wave signal from the AWG to operate the circuit in the range where the output is as low a distortion sine wave as possible.

Hardware Setup

Connect the circuit shown in Figure 1 to a breadboard.

Procedure

Configure the oscilloscope instrument to capture several periods of the two signals being measured. A plot example using Scopy is presented in Figure 3.

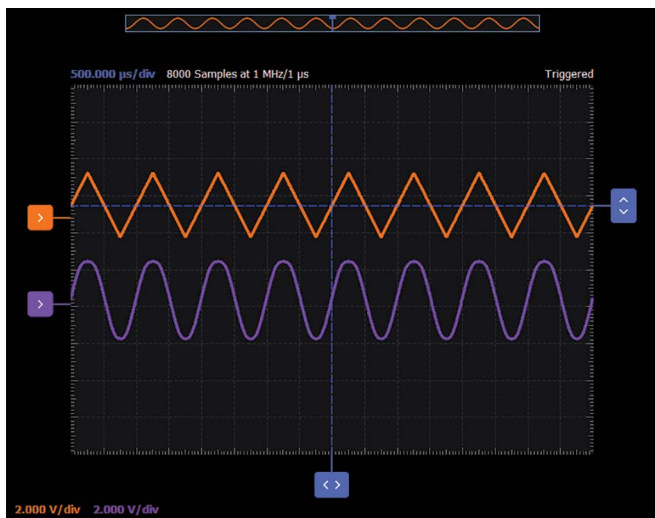


Figure 3. Differential pair triangle to sine converter Scopy plot.

Triangle Wave Generator

To make a standalone sine wave generator, we need to replace the ADALM2000 module waveform generator with a triangle wave generator. The AD654 voltage-to-frequency converter IC will be the basis of the triangle wave generator. The normal output of the AD654 is an open collector digital square wave signal. The internal timing circuit of the AD654, however, uses a ramp generator. This internal ramp waveform is available in differential form across the external timing capacitor connected to pins 6 and 7 in Figure 4. We cannot use this triangle wave signal directly without disturbing the internal timing of the AD654. We can use the AD8226 instrumentation amplifier to buffer and convert the differential signal to a single-ended signal. By adjusting the amplitude of this triangle wave signal, we can use it to drive the triangle wave to the sine wave converter circuit from Figure 1.

Materials

- ▶ Two 1 kΩ resistors
- ▶ One 47 kΩ resistor
- ▶ One 6.8 kΩ resistor
- ▶ One 220 Ω resistor
- ▶ One 5 kΩ potentiometer
- ▶ One 0.1 μF capacitor
- ▶ One 1 μF capacitor
- ▶ One red LED
- ▶ One AD654 voltage-to-frequency converter
- ▶ One AD8226 in-amp
- ▶ One small signal NPN transistor (2N3904)

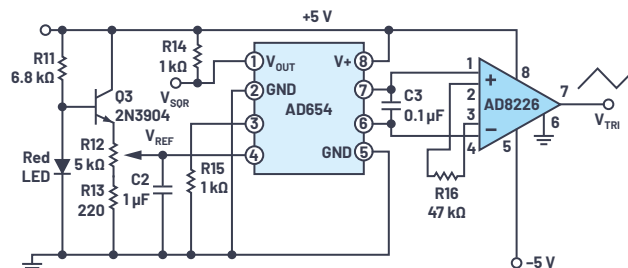


Figure 4. Voltage-to-frequency triangle wave generator.

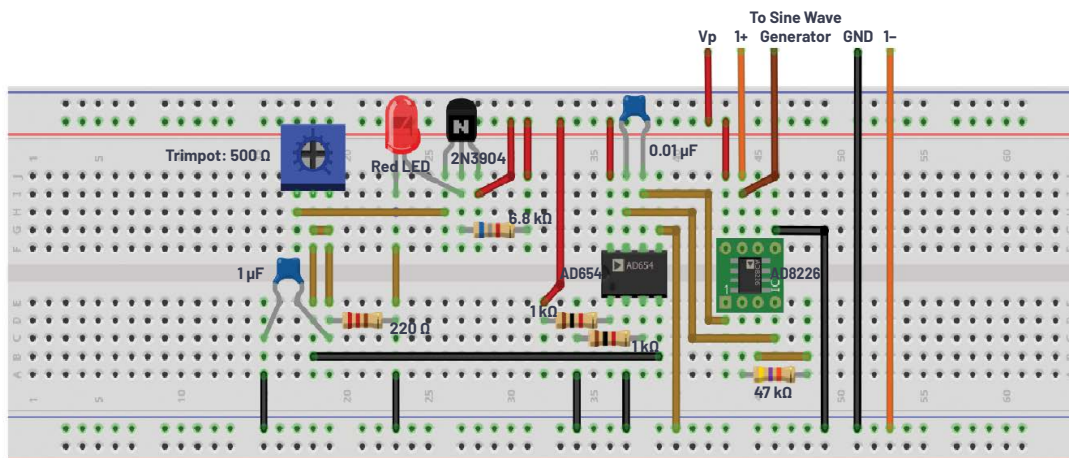


Figure 5. Voltage-to-frequency triangle wave generator breadboard connections.

When connecting the triangle wave output from the AD8226 to the input of the triangle to sine converter, replace the 2.2 kΩ fixed resistor R1 with a 5 kΩ potentiometer to adjust the signal amplitude for an optimal sine wave shape.

Hardware Setup

Connect the circuit shown in Figure 4 to a breadboard.

Procedure

With the use of ADALM2000, the output is shown in Figure 6. We can adjust the gain resistor of the in-amp (R16) so that the output of the circuit will be in the range of the in-amp supply.

In the Scopy plot in Figure 6, R16 is at 168 kΩ.

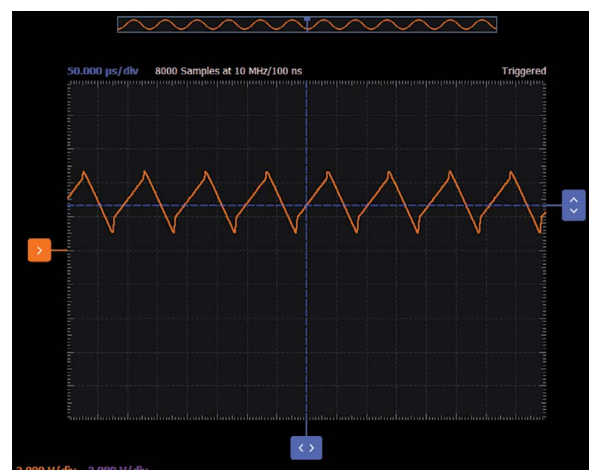


Figure 6. Voltage-to-frequency triangle wave generator Scopy plot.

Question:

- For the circuit in Figure 1, explain how the R6 potentiometer affects the output signal when set to minimum/maximum resistance value.

You can find the answer at the StudentZone blog: ez.analog.com/studentzone.



About the Author

Doug Mercer received his B.S.E.E. degree from Rensselaer Polytechnic Institute (RPI) in 1977. Since joining Analog Devices in 1977, he has contributed directly or indirectly to more than 30 data converter products and he holds 13 patents. He was appointed to the position of ADI Fellow in 1995. In 2009, he transitioned from full-time work and has continued consulting at ADI as a Fellow Emeritus contributing to the Active Learning Program. In 2016 he was named Engineer in Residence within the ECSE department at RPI. He can be reached at doug.mercer@analog.com.



About the Author

Antoni Miclaus is a system applications engineer at Analog Devices, where he works on ADI academic programs, as well as embedded software for Circuits from the Lab®, QA automation, and process management. He started working at Analog Devices in February 2017 in Cluj-Napoca, Romania. He is currently an M.Sc. student in the software engineering master's program at Babes-Bolyai University and he has a B.Eng. in electronics and telecommunications from Technical University of Cluj-Napoca. He can be reached at antoni.miclaus@analog.com.