

**Circuits
from the Lab™**
Reference Circuits

Circuits from the Lab™ reference circuits are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support visit www.analog.com/CN0281.

Devices Connected/Referenced	
ADuC7060/ADuC7061	ARM7-Based Microcontroller with Dual 24-Bit Σ - Δ ADCs
ADT7311	$\pm 0.5^{\circ}\text{C}$ Accurate, 16-Bit Digital SPI Temperature Sensor
AD8628	Precision, Low Power, Zero Drift Op Amp
ADP7102	Low Dropout Linear Regulator

Automotive SENT Interface-Based Thermocouple Temperature Sensor with Cold Junction Compensation Using the [ADuC7060/ADuC7061](#) Precision Analog Microcontroller

EVALUATION AND DESIGN SUPPORT

Design and Integration Files

[Schematic](#), [Layout Files](#), [Source Code](#)

CIRCUIT FUNCTION AND BENEFITS

This circuit uses the [ADuC7060](#) or the [ADuC7061](#) precision analog microcontroller in an accurate thermocouple temperature monitoring application. The [ADuC7060/ADuC7061](#) integrate dual 24-bit sigma-delta (Σ - Δ) analog-to-digital converters (ADCs), dual programmable current sources, a 14-bit digital-to-analog converter (DAC), and a 1.2 V internal reference, as well as an ARM7 core, 32 kB flash, 4 kB SRAM, and various digital peripherals such as UART, timers, serial peripheral interface (SPI), and I²C interfaces.

In the circuit, the [ADuC7060/ADuC7061](#) are connected to a thermocouple and a 100 Ω platinum resistance temperature detector (RTD). The RTD is used for cold junction compensation. As an extra option, the [ADT7311](#) digital temperature sensor can be used to measure the cold junction temperature instead of the RTD.

In the source code, an ADC sampling rate of 4 Hz was chosen. When the ADC input programmable gain amplifier (PGA) is configured for a gain of 32, the noise-free code resolution of the [ADuC7060/ADuC7061](#) is greater than 18 bits.

The single edge nibble transmission (SENT) interface to the host is implemented by using a timer to control a digital output pin. This digital output pin is then level shifted externally to 5 V using an external NPN transistor. An EMC filter is provided on the SENT output circuit as recommended in Section 6.3.1 of the SENT protocol (SAE J2716 Standard). The data is measured as falling edge to falling edge, and the duration of each pulse is related to the number of system clock ticks. The system clock rate is determined by measuring the SYNC pulse. The SYNC pulse is transmitted

at the start of every packet. More details are provided in the SENT Interface section.

CIRCUIT DESCRIPTION

The following features of the [ADuC7060/ADuC7061](#) are used in this application:

- A primary, 24-bit Σ - Δ ADC with a PGA. The PGA is set for a gain of 32 in the software for this application. The primary ADC was switched continuously between sampling the thermocouple and the RTD voltages.
- If an RTD is used for measuring the cold junction temperature, programmable excitation current sources force a controlled current through the RTD. The dual current sources are configurable in 200 μA steps from 0 μA to 2 mA. For this example, a 200 μA setting was used to minimize the error introduced by the RTD self-heating.
- If the [ADT7311](#) is used for measuring the cold junction temperature, the SPI interface is used in master mode to connect the [ADT7311](#) slave device.
- An internal 1.2 V reference for the ADC in the [ADuC7060/ADuC7061](#). For measuring the thermocouple voltage, the internal voltage reference was used due to its precision.
- An external voltage reference for the ADC in the [ADuC7060/ADuC7061](#). For measuring the RTD resistance, a ratiometric setup was used where an external reference resistor (R_{REF}) was connected across the external VREF+ and VREF- pins.
- The [AD8628](#) single supply op amp was used to buffer the high impedance reference voltage across R_{REF} to the ADC.
- The [OP193](#) is another option instead of the [AD8628](#).
- A DAC that was used to set the thermocouple common-mode voltage to 850 mV above ground.

Rev. A

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

- An ARM7TDMI® core. The powerful 16-/32-bit ARM7 core with integrated 32 kB flash and SRAM memory runs the user code that configures and controls the ADC, processes the ADC conversions from the RTD, and controls the communications over the SPI interface.
- Timer1 and a digital output pin are used to generate the SENT output signal.
- An optional PESDLIN protection diode for suppression of ESD, electrical fast transients (EFT), and surge transients up to 23 kV.
- An EMC filter on the SENT output as recommended in Section 6.3.1 of the SAE J2716 standard (SENT Protocol).
- Two external switches are used to force the part into its flash boot mode. By holding S1 low and toggling S2, the ADuC7060/ADuC7061 enter boot mode instead of normal user mode. In boot mode, the internal flash can be reprogrammed through the UART interface.

Both the thermocouple and the RTD generate very small signals; therefore, a PGA is required to amplify those signals. As the auxiliary ADC on the ADuC7060/ADuC7061 does not have a PGA, both were connected to the primary ADC, and switching between the two was done in software.

The thermocouple used in this application is a Type T (copper-constantan), which has a temperature range of -200°C to $+350^{\circ}\text{C}$. Its sensitivity is approximately $40\ \mu\text{V}/^{\circ}\text{C}$; therefore, in bipolar mode, the ADC, with a PGA gain of 32, can cover the entire temperature range of the thermocouple.

The RTD was used for cold junction compensation. In this circuit, a platinum, $100\ \Omega$ RTD, Enercorp PCS 1.1503.1 was used. It is available in a 0805 surface-mount package. This RTD has a temperature variation of $0.385\ \Omega/^{\circ}\text{C}$.

Note that the reference resistor, R_{REF} , should be a precision $5.6\ \text{k}\Omega$ ($\pm 0.1\%$).

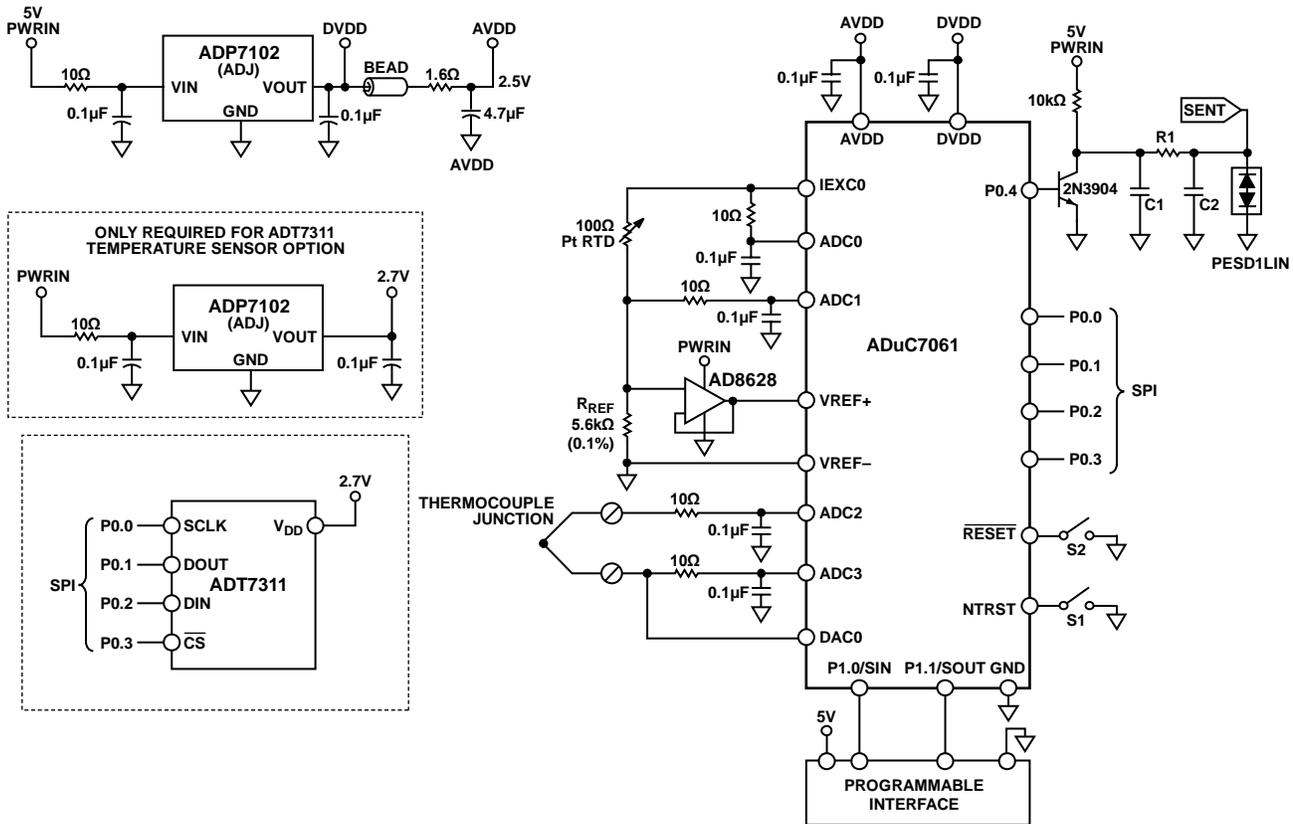


Figure 1. ADuC7060/ADuC7061 as a Temperature Monitor Controller with a Thermocouple Interface (Simplified Schematic, All Connections Not Shown)

10889-001

SENT Interface

The SENT interface is a single pin, unidirectional (sensor to host), time modulated signal used mainly in automotive systems for interfacing distributed sensors to host CPUs.

The main requirements for SENT include the following:

- It must have a 0 V to 5 V signal swing with EMC filtering.
- The clock used for the SENT signal must be accurate to $\pm 20\%$.
- The SENT output circuit must be robust enough to tolerate short circuit to ground and short circuit to supply voltages.

The associated source code uses the P0.4 digital pin of the [ADuC7061](#) as the SENT output pin. The packet format used is the single sensor packet format as detailed in A.4 section of the SAE J2716 standard (SENT Protocol) document. The source code, particularly the SENT.h and Sent.c files can be modified to support other packet formats. The overall temperature result is returned in $^{\circ}\text{C}$ format in Data Nibble 1 to Data Nibble 3. In summary, the returned output packet is

- 56 clock ticks for sync pulse
- Status pulse (7 ticks to 15 ticks)
- Data Nibble 1 (Bit 11 to Bit 8 of the temperature result)
- Data Nibble 2 (Bit 7 to Bit 4 of the temperature result)
- Data Nibble 3 (Bit 3 to Bit 0 of the temperature result)
- Data Nibble 4 (Bit 7 to Bit 4 of the counter)
- Data Nibble 5 (Bit 3 to Bit 0 of the counter)
- Data Nibble 6 (inverse of Nibble 1)

An example packet is shown in Figure 2.

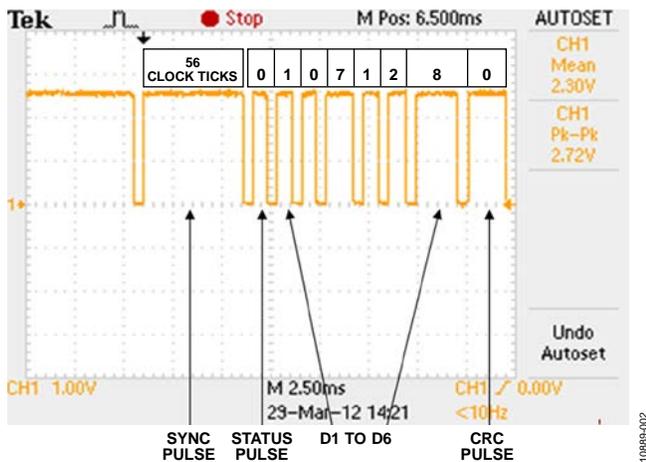


Figure 2. Example SENT Packet Measured at the P0.4 Pin

The circuit must be constructed on a multilayer printed circuit board (PCB) with a large area ground plane. Proper layout, grounding, and decoupling techniques must be used to achieve optimum performance (see [Tutorial MT-031, Grounding Data Converters and Solving the Mystery of "AGND" and "DGND,"](#) [Tutorial MT-101, Decoupling Techniques,](#) and the [ADuC7060/ADuC7061](#) evaluation board layouts).

Code Description

Timer1 is used to control the SENT output pin, P0.4. When a temperature result is been calculated from the ADC results for the thermocouple and the cold junction temperature, the SENT packet structure, SENT_PACKET, is updated, and Timer1 started. The fields of the structure are clocked out on the P0.4 pin, as shown in Figure 2. The first stage of the packet is the sync sequence. The host determines the clock period from this pulse, and it determines the subsequent nibble values from this.

To get a temperature reading, measure the temperature of the thermocouple and the RTD. The RTD temperature is converted to its equivalent thermocouple voltage via a lookup table. These two voltages are added together to give the absolute value of the voltage at the thermocouple.

First, the voltage between the two wires of the thermocouple (V_1) is measured. Then, the RTD voltage is measured and converted to a temperature via a lookup table. This temperature is then converted to its equivalent thermocouple voltage (V_2). V_1 and V_2 are then added to give the overall thermocouple voltage, and this value is then converted to the final temperature measurement.

A piecewise linearization scheme is used to calculate the final temperature value. The respective temperatures for a fixed number of voltages are stored in an array, and values in between are calculated using a linear interpolation between the adjacent points. Figure 3 gives the algorithm error using the ideal thermocouple voltages. Figure 4 shows the error obtained when using the ADC0 pin on the [ADuC7060/ADuC7061](#) to measure the 52 thermocouple voltages over the full thermocouple operating range. The overall worst-case error is $< 1^{\circ}\text{C}$.

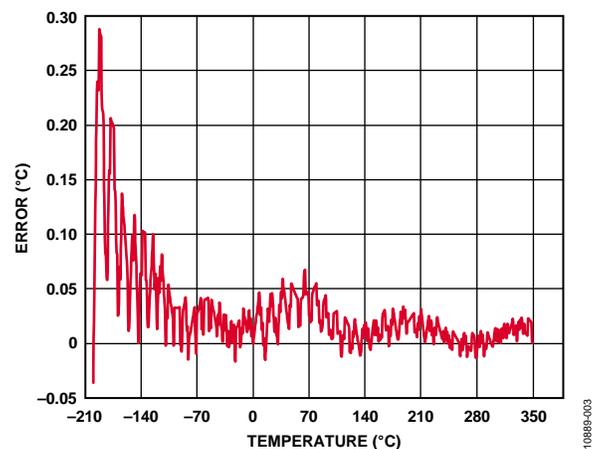


Figure 3. Error When Using Piecewise Linear Approximation Using 52 Calibration Points and Ideal Measurements

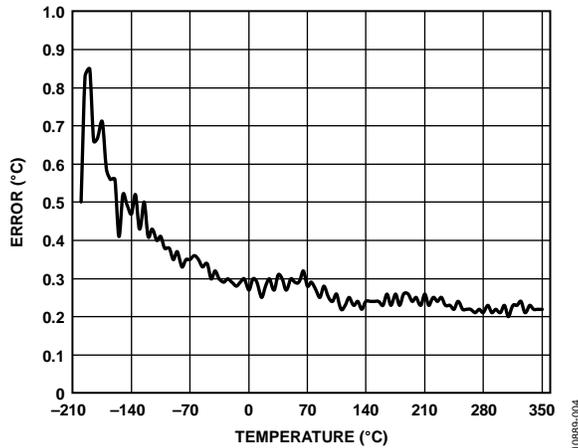


Figure 4. Error When Using Piecewise Linear Approximation Using 52 Calibration Points Measured by the ADC0 Pin of the ADuC7060/ADuC7061

The RTD temperature is calculated using lookup tables and is implemented for the RTD the same way as for the thermocouple. Note that the RTD has a different polynomial describing its temperatures as a function of resistance.

The source code in the design support package was generated using KEIL μ Vision V3.90.

For details on linearization and maximizing the performance of the RTD, refer to [Application Note AN-0970, RTD Interfacing and Linearization Using an ADuC706x Microcontroller](#).

COMMON VARIATIONS

Instead of using an external RTD, the ADT7311 temperature sensor can be used to measure the cold junction temperature.

Source code using the ADT7311 is provided with the software package in the design support package: www.analog.com/CN0281-DesignSupport.

An extra external regulator is required to power the ADT7311.

If more GPIO pins are required on the microcontroller, the ADuC7060, which comes in a 48-lead LFCSP or a 48-lead LQFP, is another option. Note that the ADuC7060/ADuC7061 can be programmed or debugged via a standard JTAG interface.

When using the external reference resistor as the reference source for the RTD measurement, it is recommended to buffer the input to the VREF+ pin using an op amp in unity-gain mode. This is to ensure that the input leakage current to the VREF+ pin does not distort the measurement accuracy. In Figure 9, the OP193 was used for this purpose. Figure 1 shows the AD8628 which is characterized to work in the -40°C to $+150^{\circ}\text{C}$ operating range.

For a wider temperature range, a different thermocouple can be used, such as a Type J. To minimize the cold junction compensation error, a thermistor can be placed in contact with the actual cold junction instead of on the PCB.

Instead of using the RTD and external reference resistor for measuring the cold junction temperature, an external digital temperature sensor can be used. For example, the ADT7311 can connect to the ADuC7060/ADuC7061 via the I²C interface.

For additional information on cold junction compensation, see the [Sensor Signal Conditioning, Analog Devices, Chapter 7, "Temperature Sensors."](#)

CIRCUIT EVALUATION AND TEST

SENT Interface Tests

The SENT interface output was evaluated using a digital oscilloscope and a logic analyzer. The SENT interface was only tested with a SENT clock period of 100 μs , which is the maximum allowed by the SENT standard. The limiting factors in this implementation include the following:

- Variation in FIQ interrupt latency for the timer. The interrupt latency of an ARM7 can be up to 45 CPU clocks. With a 10.24 MHz CPU clock, this is up to 4.4 μs . The minimum is 5 \times CPU clocks (0.5 μs). The worst-case latency occurs when the ARM7 core is executing a LDmia or STMia (load or store multiple values to/from memory). Select the **Split Load and Store Multiple** compiler option to minimize this, and see Figure 5 to see how to do this.
- The 10.24 MHz oscillator on the ADuC7060/ADuC7061 has a worst-case accuracy of $\pm 3\%$ over the -40°C to $+125^{\circ}\text{C}$ operating temperature range.

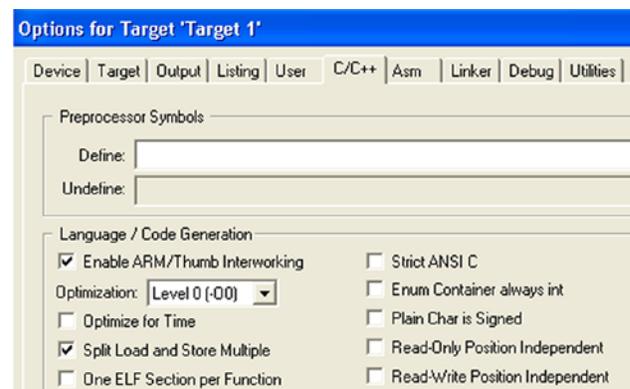


Figure 5. Selecting **Split Load and Store Multiple** Option

Despite these limitations, this implementation is well within the required $\pm 20\%$ timing accuracy of the SENT specification when a SENT clock period of 100 μs is selected.

An EMC filter has been catered for on the SENT output in Figure 1. Chose values for this filter (R1, C1, C2) to meet the targeted transmitter output waveform, as shown in Figure 6, to reduce EMC emissions due to the SENT output.

Only limited testing of this filter has been done; therefore, the resistor and capacitor values for the output filter were omitted, as is shown in Figure 1 (R1, C1, and C2).

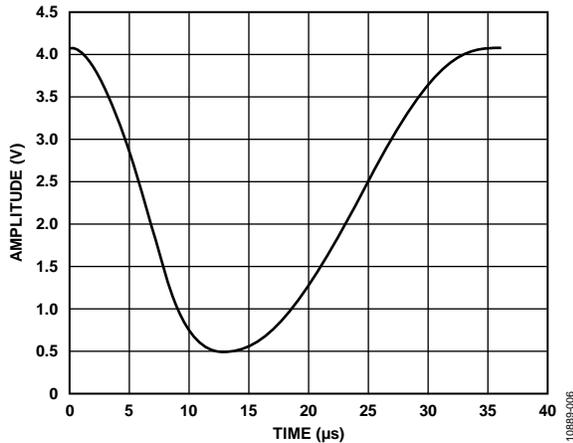


Figure 6. Example SENT Shaped Waveform Transmitter Output

To further test and evaluate the circuit, the thermocouple measurements and the RTD measurements were evaluated separately.

Thermocouple Measurement Test

The basic test setup is shown in Figure 7. Two methods were used to evaluate the performance of the circuit. Initially, the circuit was tested with the thermocouple attached to the board and used to measure the temperature of an ice bucket, and then the temperature of boiling water.

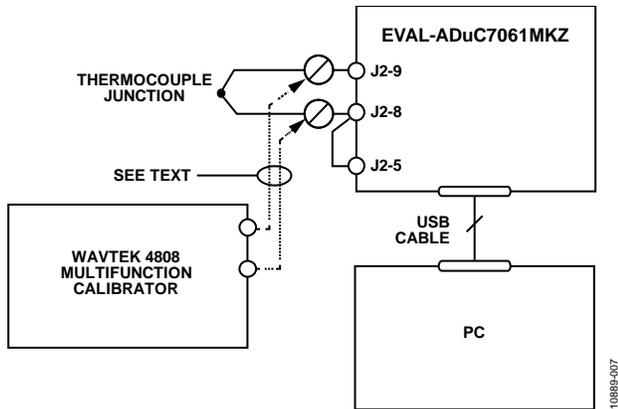


Figure 7. Test Setup Used to Calibrate and Test the Circuit Over Full Thermocouple Output Voltage Range

A Wavetek 4808 multifunction calibrator was used to fully evaluate the error, as shown in Figure 3 and Figure 4. In this mode, the thermocouple was replaced with the calibrator as the voltage source, as shown in Figure 7. To evaluate the entire range of a Type T thermocouple, the calibrator was used to set the equivalent thermocouple voltage at 52 points between -200°C to $+350^{\circ}\text{C}$ for the negative and positive ranges of the Type T thermocouple (see the ITS-90 Table for Type T thermocouple).

To evaluate the accuracy of the lookup algorithm, 551 voltage readings, equivalent to temperatures in the range of -200°C to $+350^{\circ}\text{C}$ spaced at $+1^{\circ}\text{C}$, were passed onto the temperature calculation functions. Errors were calculated for the linear method and the piecewise linear approximation method as can be seen in Figure 3 and Figure 4.

RTD Measurement Test

To evaluate the RTD circuit and linearization source code, the RTD on the board was replaced with an accurate, adjustable resistance source. The instrument used was the 1433-Z decade resistor. RTD values from $90\ \Omega$ to $140\ \Omega$, which represent an RTD temperature range of -25°C to $+114^{\circ}\text{C}$, was the range of the RTD values tested.

The error results for the RTD tests are shown in Figure 8, and the setup circuit is shown in Figure 9.

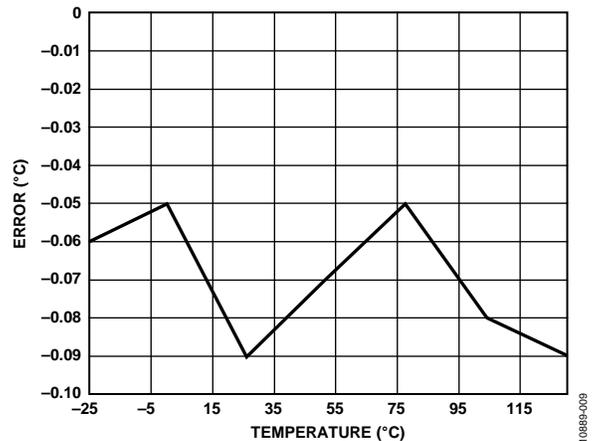


Figure 8. Error in $^{\circ}\text{C}$ of the RTD Measurement Using Piecewise Linearization Code and ADC0 Measurements

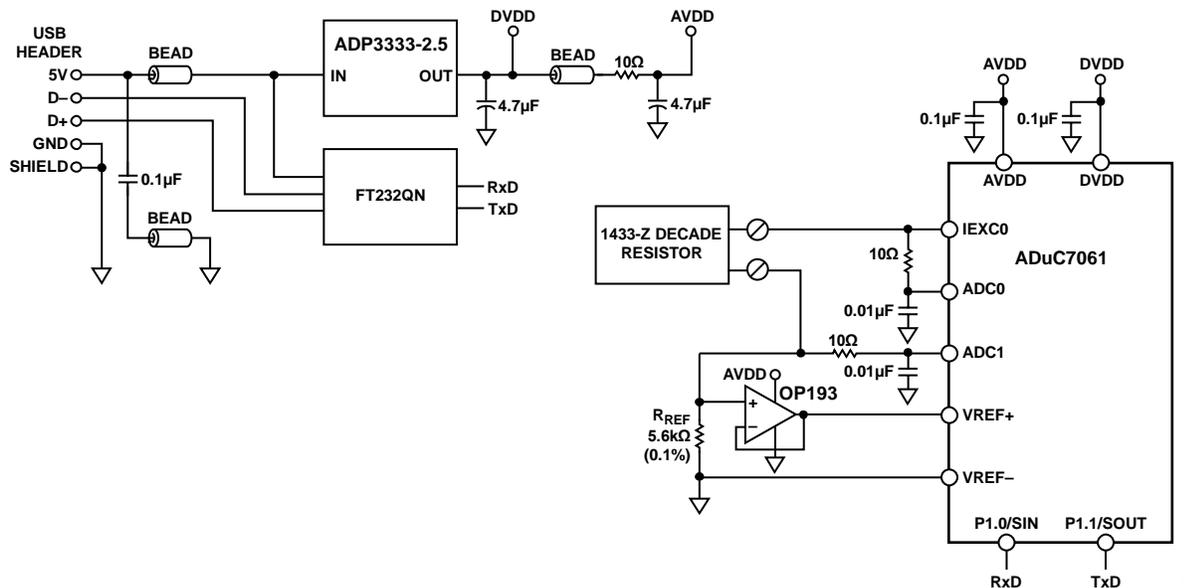


Figure 9. Test Setup Used to Calibrate and Test the RTD Output Voltage Range from -25°C to $+114^{\circ}\text{C}$

LEARN MORE

CN0281 Design Support Package:

<http://www.analog.com/CN0281-DesignSupport>.

ADIsimPower Design Tool.

Kester, Walt. 1999. *Sensor Signal Conditioning*. Analog Devices. Chapter 7, "Temperature Sensors."

Kester, Walt. 1999. *Sensor Signal Conditioning*. Analog Devices. Chapter 8, "ADCs for Signal Conditioning."

Looney, Mike. *RTD Interfacing and Linearization Using an ADuC706x Microcontroller*. AN-0970 Application Note. Analog Devices.

MT-022 Tutorial, *ADC Architectures III: Sigma-Delta ADC Basics*. Analog Devices.

MT-023 Tutorial, *ADC Architectures IV: Sigma-Delta ADC Advanced Concepts and Applications*. Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND."* Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*. Analog Devices.

ITS-90 Table for Type T Thermocouple.

SAE J2716 Standard (SENT Protocol).

Data Sheets and Evaluation Boards

[ADuC7060/ADuC7061 Data Sheet](#)

[ADuC7060/ADuC7061 Evaluation Kit](#)

[ADM3202 Data Sheet](#)

[ADT7311 Data Sheet](#)

[AD8628 Data Sheet](#)

[ADP7102 Data Sheet](#)

REVISION HISTORY

7/13—Rev. 0 to Rev. A

Change to Figure 1	2
Changes to Common Variations Section	4

7/12—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.