

Circuit Note

CN-0579

Circuits
from the Lab °
Reference Designs

Circuits from the Lab[®] reference designs are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0579.

	Devices Connected/Referenced		Devices Connected/Referenced	
	AD7768-4	4-Channel, 24-Bit, Simultaneous Sampling ADC, Power Scaling, 110.8 kHz BW	ADP1613	650 kHz /1.3 MHz Step-Up PWM DC-to-DC Switching Converter with 2.0 A Current Limit
9	AD5696R	Quad 16-Bit <i>nano</i> DAC+ with 2 ppm/°C Reference, I ² C Interface	ADP7142	40 V, 200 mA, Low Noise, CMOS LDO Linear Regulator
	ADA4807-2	3.1 nV/√Hz, 1 mA, 180 MHz, Rail-to-Rail Input/Output Amplifier	ADG5421F	\pm 60 V Fault Protection and Detection, 11 Ω RON, Dual SPST Switch
	AD8605	Precision, Low Noise, CMOS, RRIO Op Amp (single)	ADP7118	20 V, 200 mA, Low Noise, CMOS LDO Linear Regulator
	ADA4945-1	High Speed, ±0.1 µV/°C Offset Drift, Fully Differential ADC Driver	LT3092	200 mA 2-Terminal Programmable Current Source
	ADR4540	Ultralow Noise, High-Accuracy 4.096 V Voltage Reference	LT8333	Low I _Q Boost/SEPIC/Inverting Converter with 3 A, 40 V Switch

Quad-Channel IEPE Vibration Sensor Measurement System

EVALUATION AND DESIGN SUPPORT

- Circuit Evaluation Boards
 - CN0579 Circuit Evaluation Board (EVAL-CN0579-ARDZ)
- Design and Integration Files
 - Schematics, Layout Files, Bill of Materials, Software

CIRCUIT FUNCTIONS AND BENEFITS

Condition-based monitoring (CbM) enables early detection and diagnosis of machine and system abnormalities. CbM typically uses data from vibration, current, and temperature which provide key insights into the health of equipment ranging from motors and pumps to bearings and encoders. These machine health insights result in increased productivity, improved efficiency, and maximum uptime. Ultimately, by tracking the vibration analysis data over time, a fault or failure can be predicted, along with the source of the fault.

Vibration detection is the most popular method used in machine condition-based monitoring. This is done by collecting large datasets, used to identify a baseline operating condition for the equipment in both normal operating modes and failure scenarios to create an accurate understanding of the machinery. Once this information has been gathered, an algorithm or threshold detection procedure can be developed to monitor and analyze the equipment.

The reference design shown in Figure 1 is a 4-channel, high resolution, wide bandwidth, high dynamic range, integrated electronics piezoelectric (IEPE)-compatible interface data acquisition (DAQ) system that interfaces with IC piezoelectric (ICP®)/IEPE sensors. The solution provides flexible sensor interfacing to either piezoelectric or micro-electromechanical systems (MEMS) sensor with measurement capabilities that extend the frequency response to DC. The design provides four channels of full bandwidth, synchronized vibration data to the processor, where data analysis can be done locally or on a remote host over Ethernet via standard IIO framework. Large buffers of continuous data can be streamed and analyzed using standard fast Fourier transform (FFT) techniques for system characterization and machine learning algorithms.

Each channel includes an analog input protection circuitry and a software-configurable sensor bias removal circuit. Independent excitation current sources allow customized sensor options to be either enabled or disabled when connected. The board comes in an Arduino-compatible form factor that can be interfaced and powered directly from most Arduino form-factor FPGA development boards.

Circuits from the Lab[™] circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)



Circuit Note CN-0579



Figure 1. CN0579 Simplified Block Diagram

analog.com

Circuits from the Lab[™] circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page) Rev. 0 | 2 of 9

CIRCUIT DESCRIPTION

PIEZOELECTRIC VS. MEMS VIBRATION SENSORS

Piezoelectric (piezo) and MEMS are two different types of sensor technologies commonly used for measuring physical parameters such as acceleration, pressure, and temperature. The choice between these technologies can impact the way the sensor responds to different input signals, including AC and DC signals, and how it affects the frequency response.

Traditionally, piezoelectric vibration sensors have been the benchmark for vibration monitoring and are still the sensor of choice in the highest sensitivity applications, or where very high accelerations are involved. Piezo sensors are also relatively expensive and the frequency response does not extend to DC (0 Hz).

MEMS sensors were previously deemed unusable due to their limited bandwidth, g-range, and noise performance across frequency. Recent advancements in MEMS sensor technology (especially with respect to frequency response and noise performance) make MEMS sensors a viable alternative in many CbM applications. MEMS sensors are typically smaller and lower cost, and have a frequency response that extends to DC (0 Hz).

IEPE INTERFACE

The IEPE standard is a prominent signaling interface standard for today's high-end piezoelectric and MEMS sensors. The CN0579 is compatible with most IEPE vibration sensors since these sensors work on the same principle, with just some variations on the offset voltages, noise levels, bandwidths, and sensitivities.

An IEPE output signal carries both AC and DC voltages, where the vibration dependent AC voltage is DC-shifted to some voltage level typically between 7 V and 13 V. This DC level varies from sensor to sensor, and for any given sensor, it has a drift component with respect to time, temperature, and excitation current.

The IEPE sensor must be powered by a current source with a sufficiently high voltage range to fully cover the amplitude of the sensor. A typical excitation voltage of the IEPE sensors is 24 V. The CN0579 can accommodate sensors with a bias voltage up to 13 V, and a signal amplitude of 10 V p-p. The CN0579 also allows connection to voltage output vibration sensors by disabling the excitation current sources.

Input Protection

IEPE sensors are typically employed in electrically noisy industrial environments, where long sensor cables can pick up RF interference, ESD strikes, and other faults resulting in voltages outside the DAQ system's allowable input range.

The ADG5421F is an input protection switch that automatically detects overvoltage conditions and open circuits the sensor from the data acquisition signal path. For the switches to be closed, input signal voltage levels from the sensor must be within the upper and lower power supply rails by a specified voltage threshold.

The ADG5421F also provides a fault flag (FF) that can be used as an interrupt into a controller to alert the operator that an input fault has occurred. In normal operation the FF pin is pulled high, however, if either of the switches experience an over or under voltage condition, the FF is pulled low to indicate a fault has occurred.

IEPE Excitation

Take noise performance into account when creating the constant current source (CCS). Operating within signal lines as a 2-terminal current source setup, the LT3092 is well-suited for effectively driving sensors, remote supplies, and acting as a precise current limiter for local supply applications.



Figure 2. Constant Current Source

Figure 2 depicts a 2-terminal current source with Resistors R_{SET} and R_{OUT} setting the output current to 4.5 mA and Capacitor C_{SET} limiting the bandwidth of the current noise. The internal 10 μA reference current source of the LT3092 holds a stable V_{SET} across R_{SET} . The V_{SET} is mirrored across R_{OUT} , which sets the output current according to Equation 1:

$$I_{OUT}\left(A\right) = \frac{V_{SET}(V)}{R_{OUT}(\Omega)} = \frac{10\mu A \times R_{SET}(\Omega)}{R_{OUT}(\Omega)}$$
(1)

where:

 I_{OUT} is the constant current output. R_{OUT} is the current output set resistance. R_{SET} is the current input set resistance.

Note that the actual I_{OUT} current is 10 μ A larger than the output current given by Equation 1 because of the internal reference current flowing from the SET terminal.

IEPE Sensor Bias Removal

Each individual IEPE vibration sensor has an initial DC bias voltage that must be eliminated because this voltage does not carry any useful information. The CN0579 includes precision per-channel adjustable DC bias compensation that nulls out this voltage, allowing both the DC and AC content of the input signal to be accurately measured.

Figure 3 shows the DC bias removal circuitry, which can offset a sensor bias voltage up to 13 V. This voltage level shifter can

withstand a sensor offset voltage of up to 13 V and a signal swing of up to 10 V p-p, making it suitable for the majority of piezoelectric sensors. The output of the level shifter is a pseudo-differential signal referred to a 2.5 V bias (V_{OCM}), which drives the input of a fully-differential amplifier (FDA) in the following stage. A positive shifting voltage is necessary to lower the input voltage to satisfy the FDA stage input requirements, and is calculated using Equation 2:



Figure 3. IEPE Sensor Bias Voltage Correction Circuitry

$$V_{SHIFT} = \frac{V_{IEPE_SHIFTED} + G(V_{IEPE_INPUT})}{1 + G}$$
(2)

where:

 V_{SHIFT} is the required level shift voltage. $V_{IEPE_INPUT_BIAS}$ is the input bias voltage. $V_{IEPE_SHIFTED}$ is 2.52 V (must be equal to VOCM). *G* is 0.3 (computed as RF/RIN).

The AD5696R digital-to-analog converter (DAC) provides the level shift. The required digital code is calculated using Equation 3:

$$D = \frac{(V_{SHIFT} \times 2^n)}{(V_{REF} \times Gain)}$$
(3)

where:

 V_{SHIFT} is the level shift voltage. V_{REF} is the voltage reference of AD5686R. *Gain* is the gain setting of AD5686R. *D* is the digital code. *N* is the number of bits of AD5686R (16-bit).

Figure 4 shows the required V_{SHIFT} and corresponding output codes for sensor bias voltages from 0 V to 13 V. Note that the minimum input voltage is zero volts, limited by the ADG5421 VSS supply being tied to ground. For example, a sensor with a 4 V bias will be limited to 8 Vp-p.



Figure 4. Level Shifting Voltage and DAC Code vs. Sensor Bias Voltage

The internal buffer of the DAC helps in limiting voltage noise, however an additional filtering mechanism is needed to further refine the output. By default, the DAC utilizes a 2.5 V reference, it is necessary to amplify the DAC output to provide a voltage range of 0 V to 5 V. This amplification ensures compatibility with the desired voltage range.

Figure 3 illustrates the level shifting DAC with a gained output using a low-pass Sallen-Key filter configuration. The filter's cutoff frequency, which determines the range of frequencies allowed to pass through, has been intentionally set to a low value of 147.71 Hz. This specific cutoff frequency can be set using Equation 4:

$$f_C = \frac{1}{2\pi\sqrt{R1 \times R2 \times C1 \times C2}} \tag{4}$$

where:

fc is the low pass cutoff frequency.

When applying a gain to the Sallen-Key filter topology, it is crucial to consider the stability of the filter. Otherwise, there is a risk of the buffer becoming an oscillator. Another important factor in relation to stability is the quality factor (Q) of the filter, which must be taken into account for this particular function.

Maintaining a sufficiently low Q factor (below 0.707) ensures that the frequency response does not exhibit peaking at the cutoff frequency. Additionally, having a low Q factor results in gentler roll-offs that begin significantly earlier than the cutoff frequency. This characteristic is desirable for achieving high linearity across the frequency range. It is important to note that the structure becomes unstable if the Q factor becomes negative.

ANTIALIASING FILTER AND FDA

Figure 5 shows the implementation of the antialiasing filter and FDA in the CN0579. The antialiasing filter and FDA employ a differential multiple feedback low-pass structure, enabling the conversion of a single-ended signal to a differential signal. The cutoff frequency of the antialiasing filter has been specifically set to 54 kHz, which surpasses the bandwidth requirements of most vibration sensors. This filter exhibits a stopband rejection of -80 dB at 2.3 MHz.



Figure 5. FDA and ADC Interface

To optimize the SNR and utilize the full scale input range of the ADC, the gain of the FDA has been configured as 2.66. Although the FDA also amplifies the wideband noise, its impact is not as significant as the improvement in signal quality due to the gain adjustment. This is primarily because the antialiasing filter effectively constrains the wideband noise, limiting its impact.

ANALOG-TO-DIGITAL CONVERSION

The CN0579 supports simultaneous sampling through the quadchannel AD7768-4 ADC. The 4-channel architecture allows users to convert multiple sensors at once to monitor one or more assets.

This ADC utilizes a sigma-delta (Σ - Δ) modulation technique providing a resolution of 24-bits, an analog input bandwidth of 110.8 kHz, and is equipped with power scaling capabilities. Each channel of the AD7768-4 incorporates its own Σ - Δ modulator and digital filter, enabling synchronized sampling of both AC and DC signals. This feature allows for precise and accurate data acquisition, providing a dynamic range of 108 dB with a maximum input bandwidth of 110.8 kHz. Additionally, this device has a typical integral nonlinearity (INL) of ±2 ppm, an offset error of ±50 μ V, and a gain error of ±30 ppm.

The AD7768-4 supports a 5 V reference voltage and converts the differential voltage between the analog inputs, AINx+ and AINx-, into a digital output. These analog inputs can be configured as either differential or pseudo differential.

In the pseudo differential mode, one of the analog inputs (either AINx+ or AINx-) can be connected to a constant input voltage, such as 0 V, GND, AVSS, or another reference voltage. To maximize the ADC input range, it is recommended to set the common-mode voltage of the analog inputs, AINx+ and AINx-, to half of the positive supply voltage. This configuration allows for optimal utilization of the ADC's input range.

The AD7768-4 operating mode is configured via a standard SPI interface. The ADC data is output via a single-ended CMOS, 4-lane, source-synchronous, serialized interface with DRDY frame signal. The resulting 24-bit digital conversion output is in two's complement format, with the most significant bit (MSB) transmitted first. The DCLK frequency can be as high as 32 MHz, with fast edge rates. Keep traces as short as possible, and perform a signal integrity analysis of the layout.

SYSTEM PERFORMANCE

Fast Fourier Transform techniques are used to test the ADC's frequency response, distortion, and noise at the rated throughput. By applying a low distortion sine wave and analyzing the digital output using an FFT algorithm, the ADC's spectral content can be examined for frequencies outside the fundamental. Figure 6 shows the proper connection of the CN0579 to the audio analyzer for signal-to-noise (SNR), total harmonic distortion (THD), and spurious-free dynamic range (SFDR) testing.



Figure 6. CN0579 Test Setup for SNR, THD, and SFDR Analysis

With the input of 10 Vp-p from the audio precision and a 10 DC offset added, the SNR, THD, and SFDR were collected on varying frequency from 1 kHz, 20 kHz, and 40 kHz. Figure 7 shows the FFT performance of the CN0579 with 1 kHz input.



Figure 7. CN0579 FFT Performance with 1 kHz Input Signal

Figure 8 shows the calculated SNR, SFDR, and THD of all four channels at frequencies of 1 kHz, 20 kHz, and 40 kHz.





DATA PROCESSING

The ADC offers various options for power scaling, filtering, and sample rates, allowing optimization to address specific constraints such as noise levels, bandwidth requirements, and power consumption. Providing many advantages when gathering data for analysis and ultimately implementing an effective predicative maintenance strategy.

Combining the flexible options within the ADC, existing software, and available tools will help accelerate the data collection process, and performance analysis required for the application.

Raw data is captured by the platform's FPGA and stored in a DMA buffer. Data can be processed locally, or exported to higher level tools like MATLAB or Python for further analysis and development of CbM detection algorithms.

POWER ARCHITECTURE

The CN0579 incorporates an efficient power solution that enables the entire signal chain to be powered by a single 5 V or 3.3 V power rail. This optimized power arrangement simplifies the overall power distribution and ensures that the system operates effectively with a single voltage source. Figure 9 presents the complete power architecture of CN0579.



Figure 9. CN0579 Power Tree

To ensure compatibility with most Arduino form-factor FPGA development boards, the board's power solution has been specifically engineered to operate using a single 3.3 V or 5 V supply. This supply voltage is typically sourced from Arduino-compatible boards. The LT8333 DC-DC converter has the capability to boost the 5 V or 3.3 V to 26.8 V, and then the on-board ADP7142 low dropout linear regulator lowers this voltage to 26 V.

COMMON VARIATIONS

If the application requires a bandwidth greater than 110 kHz,the AD4134 ADC is an alternative with a wideband response to 162 kHz. This device has a higher sampling rate and higher overall performance.

The AD4020 and lower resolution variants are SAR ADCs suitable for applications in which custom digital filters are implemented in an FPGA.

The ADA4610-1 is suitable for use in the first stage signal conditioning and for level shifting but requires higher supply voltages for correct operation.

The ADA4807-1 and ADA4940-1 are alternatives for the ADC input antialiasing filter and driver stage.

The ADAQ7980/ADAQ7988 are 16-bit ADC μModule[®] data acquisition systems that integrate the ADC and the ADC driver stage, as well as the most critical passive components into a system in package (SiP) design. These devices are recommended where size or simplicity of implementation is more critical. These options allow the signal chain components to be selected based on performance (noise or linearity), solution size, and cost.

Analog Devices, Inc. also offers other IEPE-compatible data acquisition systems. The CN0540 is an alternative reference design for vibration sensing applications that require single channel only. The CN0582 quad-input channel DAQ is a reference design suitable for USB-based applications. For complete details, refer to the CN0540 and CN0582 circuit notes, respectively.

In systems not requiring a response down to DC (0 Hz) such as those using only piezoelectric vibration sensors, the offsetting DAC

and surrounding circuity can be eliminated. The signal chain can then be simplified to an AC-coupled inverting amplifier biased to half the ADC's reference voltage (2.5 V), with the FDA circuit left as is.

CIRCUIT EVALUATION AND TEST

This section covers the setup and procedure for evaluating the EVAL-CN0579-ARDZ. For complete setup details and other important information, refer to the CN0579 User Guide.

EQUIPMENT NEEDED

Required Hardware

- ▶ EVAL-CN0579-ARDZ circuit evaluation board
- ▶ Terasic DE10-Nano FPGA development board
- ▶ Monitor with high-definition multimedia interface (HDMI®) port
- HDMI to HDMI cable
- Wireless keyboard and mouse with USB dongle
- ▶ USB on-the-go (OTG) cable (micro USB to USB)
- Precision AC source (for example, AP2700, Brüel & Kjær, or similar precision sine generator)
- Coaxial cable with Bayonet Neill–Concelman (BNC) and subminiature version A (SMA) terminations

Required Software

- IIO Oscilloscope
- Analog Devices, Inc. Kuiper Linux image

GETTING STARTED

The basic test setup shown in Figure 10 requires the EVAL-CN0579-ARDZ to be plugged into the supported FGPA carrier board. The carrier board is required to power the EVAL-CN0579-ARDZ, run the embedded Linux image, capture the data, and display the data. Available software supports Terasic DE10-Nano and Digilent Cora Z7-07S FPGA carrier boards.



Figure 10. CN0579 Test Setup

Step by step instructions follow:

- 1. Load the Analog Devices FPGA Linux image into the microSD card.
- Configure the microSD card to use the correct files for both the EVAL-CN0579-ARDZ and the Terasic DE10-Nano carrier board.

- **3.** Connect the HDMI cable from the Terasic DE10-Nano to a monitor.
- 4. Connect the USB OTG cable to the microUSB port on the Terasic DE10-Nano, and then connect the USB dongle for the wireless mouse/keyboard.
- 5. Mount the EVAL-CN0579-ARDZ on the Terasic DE10-Nano carrier board by plugging it into the Arduino headers.
- 6. Connect the BNC end of the coaxial cable to the signal source single-ended or unbalanced output, and the other end to one of the channels of the EVAL-CN0579-ARDZ analog input SMA connector.
- 7. Using the power supply provided, connect the barrel jack to turn on the Terasic DE10-Nano.
- Set the corresponding voltage shift code for the DAC and current source control using the debug panel of the ADI IIO oscilloscope.
- **9.** Power-on the sine or arbitrary waveform generator using the following settings:
 - **a.** Set the signal type to sine wave.
 - b. Set level to 1 V p-p at 1 kHz.
 - c. Enable the output.
- **10.** Run the ADI IIO oscilloscope data capture to visualize the resulting ADC data and FFT data.

The two plots in Figure 11 and Figure 12 show the typical captures that are expected from the carrier card when configured, as described in Step 1 through Step 9. Figure 11 shows the time domain view of the ADC capture data, illustrating the expected amplitude over a number of samples.



Figure 11. Time Domain Data Capture of 1 kHz Input Signal

Figure 12 shows the same data processed and displayed as a frequency domain FFT plot.

Circuit Note



Figure 12. FFT Measurement of 1 kHz Input Signal

LEARN MORE

CN0579 Design Support Package

CN0540 Circuit Note. "24-Bit Data Acquisition System for IEPE Sensors." Analog Devices.

CN0549 Circuit Note. "Condition-Based Monitoring Development Platform." Analog Devices.

McGinley, Nial and Servis, Stuart. AN-1384 Application Note. "Pairing A Driver Amplifier with the AD7768/AD7768-4 or the AD7768-1." Analog Devices..

Moghimi, Reza. "Low Noise Signal Conditioning for Sensor-Based Circuits. ." Analog Devices.

Murphy, Chris. "Why MEMS Accelerometers Are Becoming the Designer's Best Choice for CbM Applications." Analog Devices.

DATA SHEETS AND EVALUATION BOARDS

AD7768-4 Data Sheet AD7768-4 Evaluation Board AD5696R Data Sheet AD5696R Evaluation Board ADA4807-2 Data Sheet AD8605 Data Sheet ADA4945-1 Data Sheet ADA4945-1 Evaluation Board ADR4540 Data Sheet ADP1613 Data Sheet ADP1613 Evaluation Board ADP7142 Data Sheet ADP7142 Evaluation Board ADG5421F Data Sheet ADG5421F Evaluation Board ADP7118 Data Sheet ADP7118 Evaluation Board LT3092 Data Sheet LT3092 Evaluation Board

REVISION HISTORY

11/2023—Revision 0: Initial Version



ESD Caution ESD (electrostatic discharge) sensitive device. Charged devices and circuit boards can discharge without detection. Although this product features patented or proprietary protection circuitry, damage may occur on devices subjected to high energy ESD. Therefore, proper ESD precautions should be taken to avoid performance degradation or loss of functionality.

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements or other rights of third parties that may result from their use. Analog Devices the right to change any Circuits from the Lab circuits are not but not but not do so.



©2023 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners. One Analog Way, Wilmington, MA 01887-2356, U.S.A.