
Meeting Biasing Requirements of Externally Biased RF/Microwave Amplifiers with Active Bias Controllers

by Kagan Kaya

INTRODUCTION

Radio frequency (RF) and microwave amplifiers deliver optimum performance when their biasing is well controlled. The quiescent current established by the biasing circuitry affects critical performance metrics such as linearity and efficiency. While some amplifiers are self biased, many devices require external biasing using multiple supplies that must be sequenced properly for safe operation.

This application note provides an overview of bias sequencing requirements and the effects of using various biasing schemes. It presents an elegant solution for biasing amplifiers using active bias controllers such as the [HMC980](#), [HMC980LP4E](#), [HMC981](#), [HMC981LP3E](#), and [HMC920LP5E](#).

TABLE OF CONTENTS

Introduction.....	1	Reducing the Rise Time of the V_{GATE}	
Amplifier Biasing.....	3	Voltage.....	9
Power Supply Sequencing	3	Daisy-Chain Operation.....	10
Self Biased Amplifiers.....	3	Testing the Functionality of an Active Bias	
Externally Biased Amplifiers.....	3	Controller.....	11
Cascode Amplifiers.....	4	Biasing Multiple RF Amplifiers with a Single	
Using Active Bias Controllers to Bias		Active Bias Controller.....	11
Depletion Mode RF Amplifiers.....	5	Typical Active Bias Controller Application	
Operating Principles.....	7	Circuits.....	11
Adjusting the Default V_{NEG} and V_{GATE}		Conclusion.....	16
Threshold Values.....	7		

REVISION HISTORY**12/2022—Rev. A to Rev. B**

Changes to Power Supply Sequencing Section.....	3
Changes to Self Biased Amplifiers Section.....	3
Changes to Externally Biased Amplifiers Section.....	3
Deleted Table 1; Renumbered Sequentially.....	3
Changes to HMC1131 Biasing and Sequencing Requirements Section.....	4
Changed Using Active Bias Controllers to Bias Externally Biased Amplifiers Section to Using Active	
Bias Controllers to Bias Depletion Mode RF Amplifiers Section.....	5
Changes to Using Active Bias Controllers to Bias Depletion Mode RF Amplifiers Section.....	5
Changes to Figure 10 Caption and Figure 11 Caption.....	6
Changes to Operating Principles Section.....	7
Deleted Figure 15; Renumbered Sequentially.....	7
Changes to Adjusting the Default V_{NEG} and V_{GATE} Threshold Values Section and Figure 13.....	7
Added Decreasing V_{NEG} Section.....	9
Added Increasing V_{NEG} Section.....	9
Changes to Reducing the Rise Time of the V_{GATE} Voltage Section.....	9
Changed Daisy-Chain Configuration Section to Daisy-Chain Operation Section.....	10
Changed Biasing Multiple DUTs by a Single Active Bias Controller Section to Biasing Multiple RF	
Amplifiers with a Single Active Bias Controller Section.....	11
Changes to Biasing the HMC460LC5 with the HMC981LP3E Section and Figure 25.....	11
Changes to Biasing the HMC1082LP4E with the HMC980LP4E Section and Figure 26.....	13
Changes to Biasing the HMC659LC5 with the HMC980LP4E Section and Figure 27.....	14
Changes to Figure 28.....	15
Changes to Conclusion Section.....	16

AMPLIFIER BIASING

POWER SUPPLY SEQUENCING

Power supply biasing and sequencing are critical when operating externally biased amplifiers for a number of reasons. Optimizing and controlling the bias level improves the performance of the RF amplifier and results in less part to part variation.

Device damage can result if recommended proper power supply sequencing procedures are not followed. Exceeding breakdown voltage levels can result in instant failure. Long term reliability degrades when out-of-bound conditions are repeated multiple times. This degradation can result in damage that accumulates over time, ultimately manifesting itself as a field failure.

Analog Devices, Inc., offers a wide selection of RF amplifiers. Many of these devices are designed on depletion mode, pseudomorphic, high electron mobility transfer (pHEMT) technology. The transistors used in this process typically require voltage supplies for the drain pins and gate pins. This quiescent drain current is a function of the gate voltage. See Figure 1 for the IV characteristics of a typical field effect transistor (FET) process.

 


Figure 1. Typical IV Characteristics of a Typical FET Process

As the gate to source voltage (V_{GS}) increases, more electrons enter the channel, resulting in a higher drain to source current (I_{DS}).

Additionally, as the drain to source voltage (V_{DS}) increases, the drain to source current also increases (in the linear region) due to the higher field force pulling the electrons.

In real-world amplifiers, due to effects like channel length modulation, these amplifiers can be broadly categorized into two categories: self biased and externally biased amplifiers.

SELF BIASED AMPLIFIERS

Self biased amplifiers have an internal circuit that sets the optimal bias point suitable for operation. These amplifiers tend to be best suited for broadband, low powered applications. See Figure 2 for a typical pinout of a self biased amplifier.

 


Figure 2. Typical Pinout for a Multistage Self Biased Amplifier with Multiple Bias Pins

EXTERNALLY BIASED AMPLIFIERS

Externally biased amplifiers tend to provide higher performance and more flexibility than self biased amplifiers under specific bias conditions. The quiescent drain current of the amplifier affects parameters such as power compression point, gain, noise figure, intermodulation products, and efficiency. For these high performance externally biased amplifiers, correctly sequencing the supplies is crucial for safe and optimal performance.

This procedure also applies to some other radio frequency integrated circuits (RFICs), such as frequency multipliers, upconverters, and downconverters. These products require similar biasing techniques.

Figure 3 shows the typical connections for the pins of an externally biased amplifier and the corresponding transistor pins. The pin mapping in Figure 3 is a simplified representation of the amplifier.

 


Figure 3. Typical Connections of an Externally Biased Amplifier

Many externally biased amplifiers have multiple stages to meet the required gain, bandwidth, and RF power. Figure 4 shows a typical block diagram of the HMC1131, which is a multistage externally biased amplifier.

 


Figure 4. HMC1131 Multistage Externally Biased Amplifier

HMC1131 Biasing and Sequencing Requirements

The HMC1131 is a gallium arsenide (GaAs), pHEMT, monolithic microwave integrated circuit (MMIC), medium power amplifier. It operates from 24 GHz to 35 GHz. The 4-stage design typically provides a 22 dB gain, 23 dBm output power for 1 dB compression (P1dB), and 27 dBm saturated output power (P_{SAT}) under the bias conditions of $V_{DD} = 5$ V and $I_{DQ} = 225$ mA, where V_{DD} is the drain bias voltage and I_{DQ} is the quiescent drain current. The electrical specifications table of the HMC1131 data sheet, for the 24 GHz to 27 GHz frequency range, gives this information. Figure 4 shows the pin connections of the HMC1131.

To set a target quiescent drain current (I_{DQ}) of 225 mA, set the voltage of the gate bias pins (V_{GG1} and V_{GG2}) between 0 V and -2 V. To set that negative voltage without damaging the amplifier, follow the recommended biasing sequence during power up and power down.

The recommended bias sequence during power up for the HMC1131 is the following:

1. Connect to ground.
2. Set V_{GG1} and V_{GG2} to -2 V.
3. Set V_{DD1} through V_{DD4} , the drain voltage bias pins, to 5 V.
4. Increase V_{GG1} and V_{GG2} to set an I_{DQ} of 225 mA.
5. Apply the RF signal.

The recommended bias sequence during power down for the HMC1131 is the following:

1. Turn the RF signal off.
2. Decrease V_{GG1} and V_{GG2} to -2 V to reduce I_{DQ} to 0 mA.
3. Decrease V_{DD1} through V_{DD4} to 0 V.
4. Increase V_{GG1} and V_{GG2} to 0 V.

When the gate voltage (V_{GGx}) is -2 V, the transistors are pinched off. Therefore, I_{DQ} is typically close to zero.

In general, the recommended biasing sequence is similar for most externally biased amplifiers. I_{DQ} , V_{DDx} , and V_{GGx} values are differ-

ent for different devices. For GaAs devices, V_{GG} is generally set to -2 V or -3 V to turn off the amplifier, while that voltage can be -5 V to -8 V for gallium nitride (GaN) amplifiers. Similarly, V_{DDx} can reach 28 V, even 50 V, for GaN devices, while it is usually less than 13 V for GaAs amplifiers.

In general, for multistage amplifiers, the V_{GG} pins are connected and biased together. By following the same procedure, a user can get the typical performance results provided on the data sheet. Operating the amplifier under different bias conditions may provide different performance.

Figure 5 shows the P1dB vs. the frequency at various supply currents, and Figure 6 shows the output third order intercept (IP3) performance vs. the frequency at various supply currents for the HMC1131.

 


Figure 5. P1dB vs. Frequency at Various Supply Currents

 


Figure 6. Output IP3 vs. Frequency at Various Supply Currents, $P_{OUT}/Tone = 10$ dBm

CASCODE AMPLIFIERS

Analog Devices' wideband distributed amplifiers often use a cascode architecture to extend their frequency range. The cascode distributed amplifier uses a fundamental cell of two FETs in series, source to drain. This fundamental cell is duplicated a number of

times. This duplication increases the operation bandwidth. Figure 7 shows a simplified schematic for the fundamental cell.

 


Figure 7. Simplified Fundamental Cascode Cell Schematic

With some exceptions, these cascode-based wideband amplifiers are externally biased.

The HMC637A is a wideband amplifier that uses this cascode topology. The HMC637A is a GaAs, MMIC, metal semiconductor field effect transistor (MESFET) distributed power amplifier that operates between dc and 6 GHz. Figure 8 shows the pin connections for the HMC637A.

 


Figure 8. HMC637A Pin Connections

The amplifier provides 14 dB of gain, 43 dBm of output IP3, and 30.5 dBm of output power at a 1 dB gain compression under the bias conditions of $V_{DD} = 12$ V, $V_{GG2} = 6$ V, and $I_{DQ} = 400$ mA. The electrical specifications table of the HMC637A data sheet provides more information.

To set the recommended quiescent drain current of 400 mA, V_{GG1} must be somewhere between 0 V and -2 V. To set the desired drain current, follow the recommended bias sequence during power up and power down.

The recommended bias sequence for the HMC637A during power up follows:

1. Connect to ground.
2. Set V_{GG1} to -2 V.
3. Set V_{DD} to 12 V.
4. Set V_{GG2} to 6 V (V_{GG2} can be generated using a resistor divider derived from V_{DD}).
5. Increase V_{GG1} to set a typical quiescent current (I_{DQ}) of 400 mA.

6. Apply the RF signal.

The recommended bias sequence for the HMC637A during power down follows:

1. Turn off the RF signal.
2. Decrease V_{GG1} to -2 V to set $I_{DQ} = 0$ mA.
3. Decrease V_{GG2} to 0 V.
4. Decrease V_{DD} to 0 V.
5. Increase V_{GG1} to 0 V.

USING ACTIVE BIAS CONTROLLERS TO BIAS DEPLETION MODE RF AMPLIFIERS

There are two popular approaches used to externally bias RF amplifiers:

- Constant gate voltage biasing. In this approach, the gate voltage is set to achieve the desired quiescent current (I_{DQ}). This gate voltage value is then kept constant during operation, which typically results in a variable drain current (I_{DD}) under the RF drive.
- Constant drain current biasing. In this approach, the gate voltage value is varied to achieve the desired drain current. The drain current is monitored and the gate voltage is adjusted to maintain a constant drain current for different RF drive levels. This technique is generally referred to as active bias control.

Another approach, a subset of the constant drain current approach, consists of following the constant I_{DD} approach and switching in between multiple constant I_{DD} levels when necessary due to various field scenarios. For instance, a user may bias a power amplifier for high current levels during rainy weather to compensate for the additional rain attenuation. Similarly, a user may bias the same power amplifier for low current levels during clear weather to reduce the power consumption.

Analog Devices RF amplifiers are generally characterized with a constant gate voltage, using bench top power supply units.

Designing bias circuits for amplifiers that keep the drain current constant and provide necessary sequencing can be cumbersome. Such control circuits are complicated and require not only multiple external components such as low drop out regulators (LDOs), charge pumps, voltage sequencing, and protection circuits, but also calibration cycles. Such implementations can occupy a large printed circuit board (PCB) area that is often much larger than the amplifier itself.

The HMC981LP3E, HMC980LP4E, and HMC920LP5E are 3 mm × 3 mm, 4 mm × 4 mm, and 5 mm × 5 mm plastic packaged active bias controllers. Figure 9 shows the PCB area required for a typical application, including external passive components.

 


Figure 9. PCB Area Required in Typical Application

The Analog Devices active bias controller family offers some key benefits:

- ▶ Internal voltage generators generate the required negative voltage required by depletion mode amplifiers. These generators eliminate the need for external negative voltage inverters and reduce external component count, PCB, space and system cost.
- ▶ Continuous gate voltage adjustment ensures a constant RF amplifier drain current.
- ▶ Bias accuracy improves due to the reduction of device to device variation effects. The gate voltage required to obtain a desired drain current varies from part to part. Active bias controllers adjust the gate voltage level separately for each individual device and reduce the performance difference introduced by device to device variation.

Figure 10 and Figure 11 show typical variations in drain current when constant gate voltage and constant drain current biasing are used. The plots indicate that constant drain current biasing results in smaller part to part variation in drain current and lower drift of the drain current vs. temperature.

 


Figure 10. Typical Part to Part Drain Current Variation of an RF Amplifier with Constant Gate Voltage Bias (6 Devices)

 


Figure 11. Typical Part to Part Drain Current Variation of an RF Amplifier with Constant Drain Current Bias Control from the HMC920LP5E (6 Devices)

 


Figure 12. Typical Application Circuit for the HMC980LP4E

Table 1. Selected Features of Active Bias Controllers

Device Number	Supply Range (V)	V _{DRAIN} (V)	I _{DRAIN} (mA)	I _{GATE} (mA)	Over/Under Current Alarm	Short-Circuit Protection	V _{DRAIN} LDO	Negative Voltage Generator
HMC920LP5E	5 to 16.5	3 to 15	0 to 500	-4 to +4	Yes	Yes	Yes	Yes
HMC980LP4E	5 to 16.5	5 to 16.5	50 to 1600	-4 to +4	Yes	Yes	No	Yes
HMC981LP3E	4 to 12	4 to 12	20 to 200	-0.8 to +0.8	No	Yes	No	Yes

With an internal feedback loop, the gate voltage varies to maintain a constant drain current through the amplifier under bias, independent of the temperature and amplifier threshold variations. The drain current setpoint is adjusted by an external resistor. Figure 12 shows the R_{SENSE} resistor (R10) connected to Pin 20 of the HMC980LP4E.

Further details on how to calculate the R_{SENSE} and V_{DD} values can be found on the active bias controller data sheets.

Analog Devices offers three active bias controllers: HMC920LP5E, HMC980LP4E, and HMC981LP3E. Table 1 details selected features of these active bias controllers.

The HMC980LP4E provides the ability to source high drain currents, while the HMC981LP3E is best suited for devices that require lower drain currents. In addition to the negative voltage generator, the HMC920LP5E integrates a positive voltage regulator, providing the ability to source drain pins.

OPERATING PRINCIPLES

For externally biased amplifiers, Analog Devices data sheets highlight the biasing requirements for V_{GG} and I_{DD} at the bottom of electrical specifications table. For instance, the HMC637A requires its V_{GG1} pin to be adjusted from -2 V to 0 V to obtain a typical I_{DQ} of 400 mA. In addition, the recommended power-up and power-down sequencing must be followed to avoid damaging the device.

The HMC980LP4E employs integrated control circuitry to manage safe power-up and power-down sequencing.

During power-up, the V_{DD} and V_{DIG} supplies of the bias controller turn on (V_{DIG} turns on before V_{DD}), and then the voltage on V_{NEG} is generated by the internal negative voltage generator (NVG). V_{NEG} starts to decrease and stops when it reaches its default value (typically -2.46 V). The V_{GATE} output voltage also starts to decrease, following V_{NEG} . When $V_{\text{NEG}} = -2.46$ V and $V_{\text{GATE}} = -2.1$ V, the V_{DRAIN} output pin is enabled, and V_{GATE} begins to increase toward 0 V until the setpoint I_{DD} value is reached.

Similar power-down protection circuitry also provides safe power-down. During power-down, the V_{GATE} output pin always shuts down after the V_{DD} pin, even if there is a short circuit on the V_{DD} pins or on the V_{GGx} pins of the HMC637A amplifier. This feature introduces advanced protection of the amplifier, under excessive drain current scenarios.

ADJUSTING THE DEFAULT V_{NEG} AND V_{GATE} THRESHOLD VALUES

The default value for V_{NEG} (-2.46 V) is shown in Figure 13. Due to the internal logic that exists inside the HMC980LP4E, this value of the V_{NEG} voltage limits the V_{GATE} output voltage range of the HMC980LP4E. With the default configuration, the typical V_{GATE} output swing is between -2.1 V and 0 V. That is, there is approximately

400 mV of headroom between V_{NEG} and the most negative voltage that V_{GATE} can reach.

 


Figure 13. Default V_{NEG} Value

For some RF amplifiers, gate voltages that are more negative than -2.1 V are required. Also, some RF amplifiers have a gate voltage absolute maximum rating (AMR) that is greater (more positive) than -2.1 V. The default value of V_{NEG} (-2.46 V) and the V_{GATE} threshold value ($V_{GATE_THRESHOLD} = -2.1$ V) can be adjusted using external resistors ($R5$, $R6$, $R7$, and $R8$) as shown in Figure 14 ($V_{GATE_THRESHOLD}$ is the voltage at which the negative going V_{GATE} reaches its most negative value and starts tending positive).

 


Figure 14. External Resistors for Adjusting Default V_{NEG} and V_{GATE} Values

V_{NEG} can be either decreased or increased relative to its default value. As V_{NEG} is adjusted, the value of $V_{GATE_THRESHOLD}$ must also be adjusted and at least 0.3 V greater (more positive) than V_{NEG} . For example, if V_{NEG} is to be reduced to -2.5 V, $V_{GATE_THRESHOLD}$ must be reduced to -2.2 V or greater (more positive). The external resistors for setting V_{NEG} and $V_{GATE_THRESHOLD}$ are set according to the following equations.

Decreasing V_{NEG}

If the desired $V_{NEG} < -2.46$ V,

$R5$ (k Ω) = open

$$R6 \text{ (k}\Omega\text{)} = \frac{50}{\left(50 \times \frac{V_{NEG_DESIRED} - 0.815}{262 \times (0.815 - V_{REF})}\right) - 1} \quad (1)$$

$R7$ (k Ω) = open

$$R8 \text{ (k}\Omega\text{)} = \frac{50}{\left(50 \times \frac{V_{GATE_THRESHOLD} - 0.815}{262 \times (0.815 - V_{REF})}\right) - 1} \quad (2)$$

where V_{REF} is 1.44 V. For example, if the desired V_{NEG} is -3.2 V, set $V_{GATE_THRESHOLD}$ to -2.9 V.

$R6 = 221$ k Ω , $R8 = 372$ k Ω , and $R5 = R7 =$ open.

Increasing V_{NEG}

If the desired $V_{NEG} > -2.46$ V,

$R6$ (k Ω) = open

$$R5 \text{ (k}\Omega\text{)} = \frac{262}{\left(262 \times \frac{V_{REF} - 0.815}{50 \times (0.815 - V_{NEG})}\right) - 1} \quad (3)$$

$R8$ (k Ω) = open

$$R7 \text{ (k}\Omega\text{)} = \frac{262}{\left(262 \times \frac{V_{REF} - 0.815}{50 \times (0.815 - V_{GATE_THRESHOLD})}\right) - 1} \quad (4)$$

where $V_{REF} = 1.44$ V. For example, if the desired $V_{NEG} = -1.5$ V, set $V_{GATE_THRESHOLD}$ to -1.2 V.

$R5 = 631$ k Ω , $R7 = 419$ k Ω , and $R6 = R8 =$ open.

Equation 3 and Equation 4 can also be used to adjust the V_{NEG} and $V_{GATE_THRESHOLD}$ voltages on the HMC981LP3E and the HMC920. For the HMC981LP3E, the default value for V_{NEG} is -2.5 V and V_{REF} is equal to 1.42 V. For the HMC920, the default value for V_{NEG} is -2.5 V and V_{REF} is equal to 1.5 V.

REDUCING THE RISE TIME OF THE V_{GATE} VOLTAGE

A delay exists between the enable signal and the settling of V_{GATE} . This delay is due to a combination of the internal propagation delay of the bias controller and the settling time of the V_{GATE} voltage. The V_{GATE} settling time is affected by the shunt capacitors used on the connection between the VGATE output pin of the active

bias controller pin and the VGG1 input pin of the RF amplifier. The HMC980LP4E typical enable waveform (see Figure 15) shows a V_{GATE} settling time of greater than 1 ms.

 


Figure 15. HMC980LP4E Typical Enable Waveform

The external circuitry affects the V_{GATE} rise time but not the propagation delay. Figure 16 shows a typical connection between the HMC980LP4E and an RF amplifier. Generally, a shunt capacitor is added to the VGG1 pin of the RF amplifier. For stability, a resistor is sometimes placed in series with this capacitor ($R1$ in Figure 16).

 
 
 
 
 


Figure 16. V_{GATE} Connection Circuitry Between the HMC980LP4E and the DUT

When $C1 = 10$ μ F and $R1 = 0$ Ω , the typical rise time is greater than 1.5 ms (see Figure 17). Reducing $C1$ to 1 μ F reduces the rise time to 131 μ s (see Figure 18).

Figure 17. Typical V_{GATE} Rise Time with $C1 = 10 \mu F$ Figure 18. Typical V_{GATE} Rise Time with $C1 = 1 \mu F$

When $C1 = 100 \text{ nF}$, the V_{GATE} rise time is reduced to $15.5 \mu s$, but the signal has overshoot and ringing (see Figure 19). Adding a series resistor, $R1$, with a value of 68Ω (with $C1$ equal to 100 nF) improves the response and keeps the rise time within a similar level (see Figure 20).

Figure 19. Typical V_{GATE} Rise Time with $C1 = 100 \text{ nF}$ Figure 20. Typical V_{GATE} Rise Time with $C1 = 100 \text{ nF}$ and $R1 = 68 \Omega$

DAISY-CHAIN OPERATION

Where multiple active bias controllers are controlling multiple cascaded RF amplifiers, they can be used in a daisy-chain configuration. The TRIGOUT output of the active bias controller activates when the V_{DRAIN} , V_{G2} , and V_{GATE} output voltages settle. Using the TRIGOUT signal to enable another bias controller with the enable pin (EN) improves system safety. A daisy-chain configuration has many applications. Figure 21 and Figure 22 show two applications. The number of amplifier stages and bias controllers can be increased.

 


Figure 21. Daisy-Chain Configuration with Two Amplifiers in Cascade Configuration

 


Figure 22. Daisy-Chain Configuration Where Amplifiers Are in Different Signal Paths

Figure 23 shows the V_{DRAIN} and V_{GATE} responses of two active bias controllers in a daisy-chain configuration, powering two amplifiers individually. The second bias controller is enabled by the trigger

signal from the first bias controller. This architecture ensures that the second amplifier enables after the first.

 


Figure 23. V_{DRAIN} Responses of Two Active Bias Controllers in a Daisy-Chain Configuration, Powering Two Amplifiers Individually

 


Figure 24. V_{GATE} Responses of Two Active Bias Controllers in a Daisy-Chain Configuration, Powering Two Amplifiers Individually

TESTING THE FUNCTIONALITY OF AN ACTIVE BIAS CONTROLLER

Without the active bias controller connected to an RF amplifier and operating in a closed loop, it is difficult to test the device's full functionality. However some useful diagnostic checks can be carried out on the standalone device.

- ▶ When $I_{DD} = 0$ mA, there must be a negligible voltage drop across between the V_{DD} input pin and the V_{DRAIN} output pin. Therefore, V_{DRAIN} must be almost equal to V_{DD} .

- ▶ V_{NEG} is typically -2.46 V.
- ▶ V_{GATE} hits a maximum value of $V_{NEG} + 4.5$ V, which is typically 2.04 V.

These numbers apply to [HMC980](#) (die and packaged versions). For the [HMC981](#) (die and packaged versions) and [HMC920LP5E](#) controllers, the correct values can be obtained from the device data sheets.

BIASING MULTIPLE RF AMPLIFIERS WITH A SINGLE ACTIVE BIAS CONTROLLER

It is possible to bias two or more amplifiers using a single active bias controller. To do so, calculate the R_{SENSE} value based on the total combined drain current of the two amplifiers.

Note, however, that using this approach limits the benefits that an active bias controller offers for the following reasons:

- ▶ An active bias controller is not able to compensate device-to-device gate voltage variation that is common with GaAs devices. As a result, two devices that are being biased using one gate voltage, may have different drain currents (the gate voltage is adjusted so that the combined drain currents are equal to the setpoint current).
- ▶ If one of the amplifiers draws excessive current due to a short circuit or other failure mechanisms, the bias controller shuts down all amplifiers under bias. Although this does not damage the devices, it limits system functionality.

TYPICAL ACTIVE BIAS CONTROLLER APPLICATION CIRCUITS

Biasing the HMC460LC5 with the HMC981LP3E

To bias the [HMC460LC5](#) with the [HMC981LP3E](#), do the following:

- ▶ Set R_{10} to 426Ω to set $I_{DD} = 75$ mA for the [HMC981LP3E](#). Use a standard resistor value of 430Ω , which results in a V_{DD} value of 8.75 V.
- ▶ Use R_4 and R_6 to ensure that the V_{GATE} voltage is within the Absolute Maximum Ratings section of the [HMC981LP3E](#) data sheet. Refer to the [Adjusting the Default \$V_{NEG}\$ and \$V_{GATE}\$ Threshold Values](#) section for details.
- ▶ The shunt V_{GG} capacitor values can be reduced to increase the rise time (see [HMC460LC5](#) in [Figure 25](#)). Refer to the [Reducing the Rise Time of the \$V_{GATE}\$ Voltage](#) section for further details.

Figure 25. Application Circuit for Biasing the HMC460LC5 with the HMC981LP3E

Biasing the HMC1082LP4E with the HMC980LP4E

To bias the [HMC1082LP4E](#) with the [HMC980LP4E](#), do the following:

- Set R10 to 680 Ω to set $I_{DD} = 220$ mA for the HMC980LP4E, which results in a V_{DD} value of 5.62 V.
- Use R5 and R7 to ensure that the V_{GATE} voltage is within the Absolute Maximum Ratings section of the HMC980LP4E data

sheet. Refer to the [Adjusting the Default VNEG and VGATE Threshold Values](#) section for details.

- The shunt V_{GG} capacitor values can be reduced to increase the rise time (see the HMC1082LP4E in [Figure 26](#)). Refer to the [Reducing the Rise Time of the VGATE Voltage](#) section for further details.

 


Figure 26. Application Circuit for Biasing the HMC1082LP4E with the HMC980LP4E

To bias the [HMC659LC5](#) with the [HMC980LP4E](#), do the following:

- ▶ Use R5 and R7 to ensure that the VGATE voltage is within the Absolute Maximum Ratings section of the [HMC980LP4E](#) data sheet. Refer to the [Adjusting the Default VNEG and VGATE Threshold Values](#) section for further details.
- ▶ The shunt V_{GGX} capacitors value can be reduced to increase the rise time (see [HMC659LC5](#) in [Figure 27](#)). Refer to the [Reducing the Rise Time of the VGATE Voltage](#) section for further details.

$$V_{DD} = V_{DRAIN} (8V) + I_{DRAIN} (0.3A) \times R_{DS_ON} (2.8\Omega) = 8.84V$$

 


Figure 27. Application Circuit for Biasing the HMC659LC5 with the HMC980LP4E

Biasing the HMC659LC5 with the HMC920LP5E

To bias the [HMC659LC5](#) with the [HMC920LP5E](#), do the following:

- ▶ Set R_{SENSE} to 549 Ω to set $I_{\text{DD}} = 300 \text{ mA}$ for the [HMC920LP5E](#).
- ▶ Set R_8 to 30.9 k Ω to set $V_{\text{DRAIN}} = 8 \text{ V}$.
- ▶ Use R_{20} and R_{22} to ensure that the V_{GATE} voltage is within the Absolute Maximum Ratings section of the [HMC920LP5E](#) data

sheet. Refer to the [Adjusting the Default VNEG and VGATE Threshold Values](#) section for details.

- The shunt V_{GGX} capacitor values can be reduced to increase the rise time (see **HMC659LC5** in **Figure 28**). Refer to the **Reducing the Rise Time of the VGATE Voltage** section for further details.

 


Figure 28. Application Circuit for Biasing the HMC659LC5 with the HMC920LP5E

CONCLUSION

Operating RF amplifiers with an active bias controller ensures correct on or off sequencing and reduces amplifier to amplifier variability.

The active bias controller family from Analog Devices addresses the biasing requirements of externally biased RF or microwave

components, such as FETs, amplifiers, multipliers, optical modulator drivers and frequency converters that operate on drain voltages and drain currents of 16.5 V and 1.6 A respectively. These devices offer significant configurability in terms of voltage and current ranges, alarm thresholds and response time.