

Self-Powering Through the Isolation Barrier

The isolated capacitive coupling through the lead frame plus internal rectifiers provides the isolated power source, V_{PW} . This source can be modeled as an equivalent 5.3V to 6.5V source with a 100k Ω source impedance. Hence, the power delivery to the isolated side is about 20 μ A to 32 μ A of current at 3.3V. Normally this current charges the external capacitor on V_{PW} . When the comparator and V_{REG} reference switch on, power is drawn from this capacitor for 110 μ s. The comparator will not compare again until the voltage on this capacitor recharges back to 3.3V. Since some applications need to amplify sensors or capture peak values between samples, external micropower circuitry can be powered continuously from V_{PW} as long as the

current is below 20 μ A. For example, Figure 2 shows a thermocouple that is amplified and cold-junction compensated using continuous power from V_{PW} . Figure 3 detects overcurrent through an AC line sense resistor, where the LTC1531 provides both isolation and DC power for the peak detect circuit. The overcurrent value trips at 1.25V at the input to the comparator, or at 125mV across R_{SENSE} .

Conclusion

The LTC1531 provides both isolated power and isolated sensing capability. This combination simplifies the design of many control functions that require high voltage isolation without having to design an isolated power supply for the sensors.

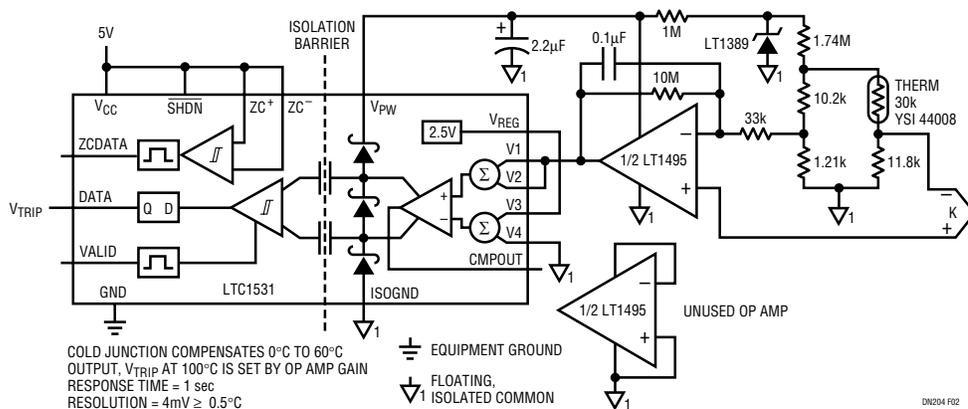


Figure 2. Overtemperature Detect

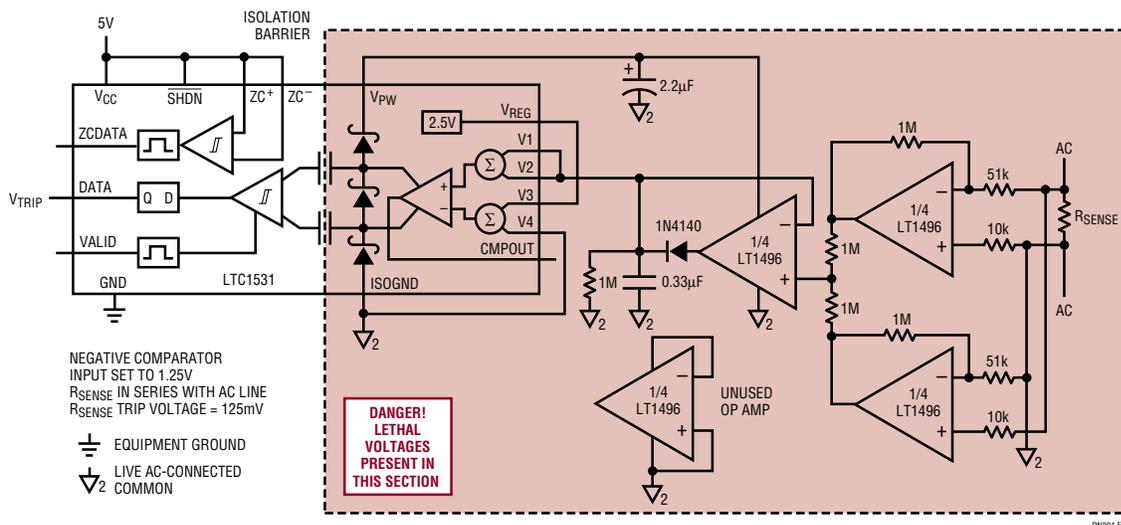


Figure 3. AC Line Overcurrent Detect

Data Sheet Download

<http://www.linear-tech.com/go/dnLTC1531>

For literature on our Comparators, call **1-800-4-LINEAR**. For applications help, call (408) 432-1900, Ext. 2456