

Maxim > Design Support > Technical Documents > Application Notes > Power-Supply Circuits > APP 1875

Keywords: charge pump, DC-DC converter, inverter, inverting power supply, dc to dc, convertors

APPLICATION NOTE 1875 Triple Capacitive Voltage Inverter with the MAX871

By: Len Sherman Feb 03, 2003

Abstract: A -3X voltage inverter is made with a SOT charge-pump IC and diode-capacitor network. Up to -15V at 10mA can be generated from 5V.

This design idea is based on a customer request for a cheap, and not very accurate, negative voltage supply of about -12V to -15V with a low output current of < 5mA and an input voltage of 5V. This application might be used for negative op-amp supply. **Figure 1** shows the typical operation circuit with the flying capacitor C1 and C2. The output voltage on pin 1 is $-V_{IN}$. Four additional capacitors (C3 to C6) and four additional diodes (D1 to D4) triple the negative output voltage at the OUT pin from $-V_{IN}$ to $-3V_{IN}$. C5 and C6 decreases the voltage with every step by $-V_{IN}$. Without any diode voltage drop C3 got $-2V_{IN}$ and C4 charges ideally to $-3V_{IN}$. It is possible to add more of these cascades but with every step the voltage drop of the diodes will reduce the effort.



Figure 1. Triple voltage inverter with MAX871.

The schematic of the design idea has been tested with 4.5V and 5V input voltage. **Figure 2** shows load current vs. output voltage. The general voltage drop on V_{OUT} is caused by the forward voltage of the external diodes of typically 0.3V to 0.4V per diode, depending on the load current. V_{OUT} is:

 $V_{OUT} = -3 \times V_{IN} + 4 \times V_{D}$

V_D: typically 0.3V to 0.4V

 V_{IN} is the input voltage on pin 2. V_D is the forward voltage drop of diode D1 to D4. If Schottky diodes are used V_D is typically 0.3V to 0.4V.



Figure 2. Load current vs. output voltage.

Component List		
C1 - C6	470nF ceramic	
C input	10µF	
D1 - D4	BAT41	

A similar version of this article appeared in the October 25, 2001 issue of *Electronic World* and *Wireless World* magazine.

Related Parts		
MAX871	Switched-Capacitor Voltage Inverters	Free Samples

More Information

For Technical Support: http://www.maximintegrated.com/support For Samples: http://www.maximintegrated.com/samples Other Questions and Comments: http://www.maximintegrated.com/contact

Application Note 1875: http://www.maximintegrated.com/an1875 APPLICATION NOTE 1875, AN1875, AN 1875, APP1875, Appnote1875, Appnote 1875 Copyright © by Maxim Integrated Products Additional Legal Notices: http://www.maximintegrated.com/legal