



Figure 2 shows this flyback converter reaching 90.5% peak efficiency. Even with no optocoupler, load regulation at various input voltages remains tight, typically 2% to 3%, as shown in Figure 3.

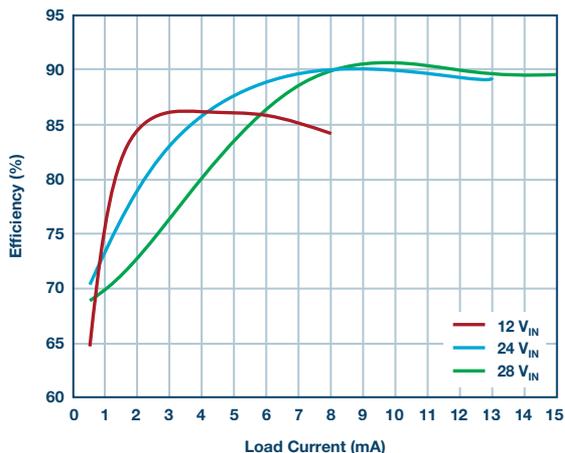


Figure 2. Efficiency of Figure 1 at various input voltages.

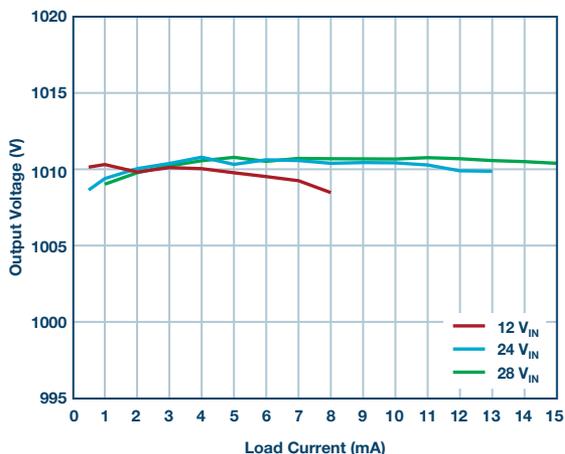


Figure 3. Load regulation of Figure 1 at various input voltages.

### 800 V/10 mA Output, from 4 V to 18 V Input

Figure 4 shows a complete 4 V to 18 V input to 800 V output solution capable of providing up to 10 mA output current. This flyback converter achieves 88.2% peak efficiency when the input is 18 V and the load current is 10 mA. Figure 5 shows the efficiency curve at various input voltages; Figure 6 shows the excellent load regulation. This solution also features a low component count.

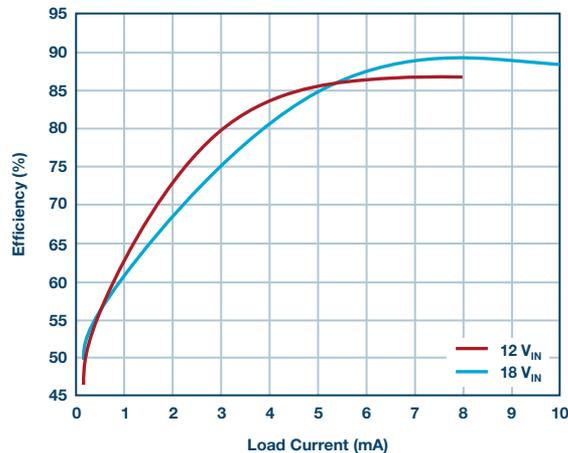


Figure 5. Efficiency of the solution in Figure 4 at various input voltages.

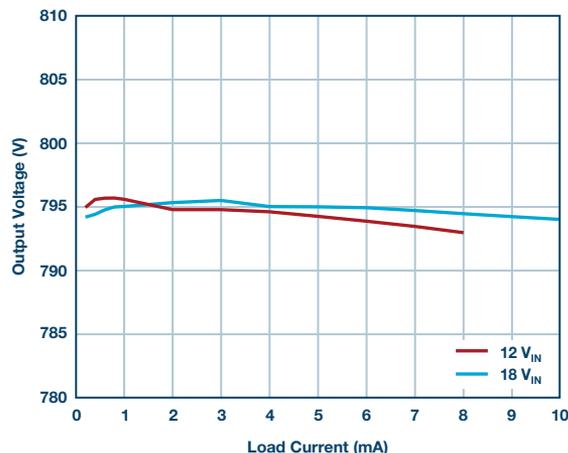


Figure 6. Load regulation of the solution in Figure 4 at various input voltages.

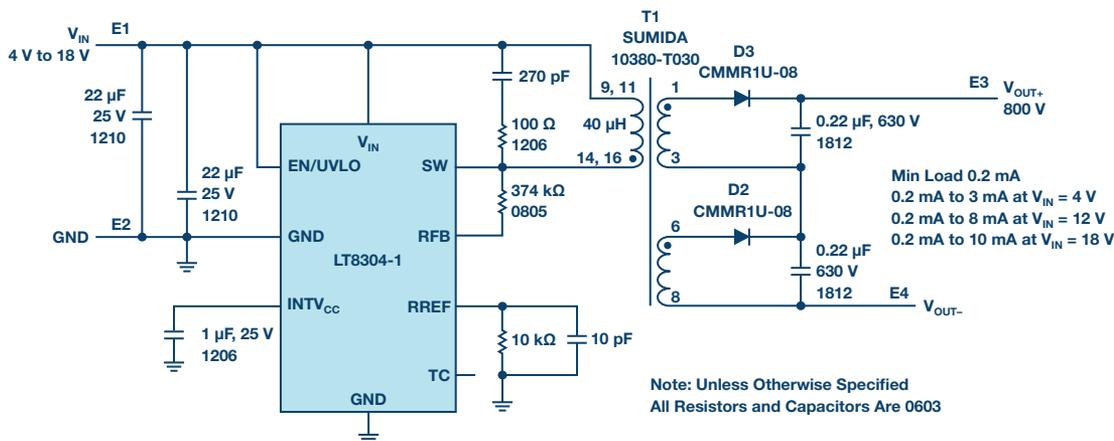


Figure 4. A complete 800 V/10 mA isolated flyback converter from a 4 V to 18 V input.

## Conclusion

The LT8304-1 is an easy to use monolithic micropower isolated flyback converter optimized for high output voltage applications. By sampling the isolated output voltage directly from the primary side flyback waveform, complete solutions maintain tight regulation—requiring neither an output voltage divider nor an opto-isolator.

The output voltage is simply programmed with two external resistors and a third optional temperature compensation resistor. Boundary mode operation enables a small magnetic solution with excellent load regulation. A 2 A, 150 V DMOS power switch is integrated, along with all the high voltage circuitry and control logic, in a thermally enhanced 8-lead SO package. The LT8304-1 operates at an input voltage range of 3 V to 100 V, and delivers up to 24 W of isolated output power.

## About the Authors

Zhijun (George) Qian is a senior engineer at Analog Devices, Inc. He is responsible for power products applications of various nonisolated and isolated converters. He obtained his B.S. and M.S. from Zhejiang University, and his Ph.D. from University of Central Florida, all in power electronics. He joined Linear Technology (now part of ADI) in 2010. He can be reached at [zhijun.qian@analog.com](mailto:zhijun.qian@analog.com).

Michael Wu is a product applications engineer at Analog Devices, Inc. He works in the Power Group focusing on isolated and nonisolated dc-to-dc converters. He studied electrical engineering at California Polytechnic State University, San Luis Obispo (B.S. and M.S.). He can be reached at [michael.wu@analog.com](mailto:michael.wu@analog.com).

## Online Support Community



Engage with the Analog Devices technology experts in our online support community. Ask your tough design questions, browse FAQs, or join a conversation.

Visit [ez.analog.com](http://ez.analog.com)

### Analog Devices, Inc. Worldwide Headquarters

Analog Devices, Inc.  
One Technology Way  
P.O. Box 9106  
Norwood, MA 02062-9106  
U.S.A.  
Tel: 781.329.4700  
(800.262.5643, U.S.A. only)  
Fax: 781.461.3113

### Analog Devices, Inc. Europe Headquarters

Analog Devices GmbH  
Otto-Aicher-Str. 60-64  
80807 München  
Germany  
Tel: 49.89.76903.0  
Fax: 49.89.76903.157

### Analog Devices, Inc. Japan Headquarters

Analog Devices, KK  
New Pier Takeshiba  
South Tower Building  
1-16-1 Kaigan, Minato-ku,  
Tokyo, 105-6891  
Japan  
Tel: 813.5402.8200  
Fax: 813.5402.1064

### Analog Devices, Inc. Asia Pacific Headquarters

Analog Devices  
5F, Sandhill Plaza  
2290 Zuchongzhi Road  
Zhangjiang Hi-Tech Park  
Pudong New District  
Shanghai, China 201203  
Tel: 86.21.2320.8000  
Fax: 86.21.2320.8222

©2018 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners. Ahead of What's Possible is a trademark of Analog Devices.  
DN20293-0-6/18

[analog.com](http://analog.com)



AHEAD OF WHAT'S POSSIBLE™