

Maxim > Design Support > Technical Documents > Application Notes > Wireless and RF > APP 2874

Keywords: rf, rfic, Ina, bias, wireless, ism, ghz, gain, noise figure, linearity, ip3, iip3, return loss, 802.11, wlan, ieee

APPLICATION NOTE 2874

2.5GHz LNA with Gain Step for 802.11b/g and Bluetooth Applications

Nov 21, 2003

Abstract: This application note presents the design of an LNA at 2.45 GHz for WLAN applications meeting 802.11b/g needs. It presents curves that show gain, noise figure, input and output return loss, and linearity.

The MAX2645 is a Silicon Germanium (SiGe) Low-Noise Amplifier (LNA) that features a 25dB gain step, shutdown mode, and adjustable IP3. The LNA has been optimized to improve the sensitivity of CMOS receivers for 2.4GHz, 802.11b and 802.11g applications. The device features +18.7dB of gain, a noise figure of 1.9dB, and an Input IP3 of +0.5dB in High-Gain Mode. In Low-Gain Mode, the LNA has -7.0dB of insertion loss and an Input IP3 of +15.3dB. Supply current is a low 8.9mA in High-Gain Mode, 2.7mA in Low-Gain Mode and typically 0.1uA in Shutdown Mode. The LNA also features an externally adjustable bias control, set with a single resistor, which allows the user to meet minimum linearity



Click here for an overview of the wireless components used in a typical radio transceiver.

requirements while minimizing current consumption. Table 1 below summarizes MAX2645 performance. The schematic for optimizing the MAX2645 for 2.45GHz is represented in **Figure 1**. **Figures 2-6** demonstrate High-Gain, and Low-Gain performance of the LNA versus frequency. For further information, consult the MAX2645 SiGe LNA and MAX2645 EV kit datasheets.

Table	1.	MAX2645	SiGe	LNA	Pert	ormance	

Mode	e Supply Current (mA)	Gain (dB)	Noise Figure (dB)	Input IP3 (dBm)		Output Return Loss (dB)
High Gain	8.9	+18.7	1.9	+0.5	-8.3	-15.2
Low- Gain	2.7	-7.0	14.1	+15.3	-11.3	-8.5

(f = 2.45GHz, V_{CC} = 3.0V, R_{BIAS} = 20k Ω)

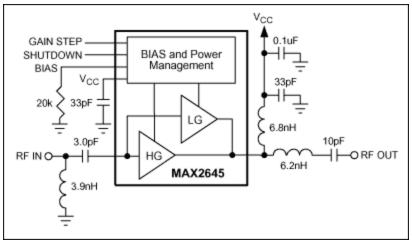


Figure 1. MAX2645 SiGe LNA 2.45GHz LNA schematic.

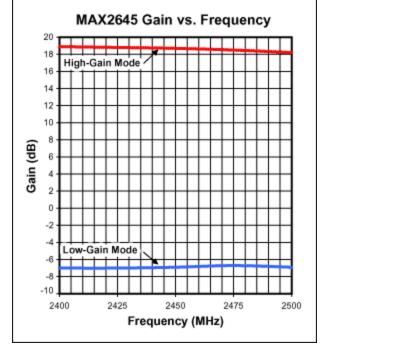


Figure 2. MAX2645 Gain versus frequency ($V_{CC} = 3.0V$, $R_{BIAS} = 20k\Omega$).

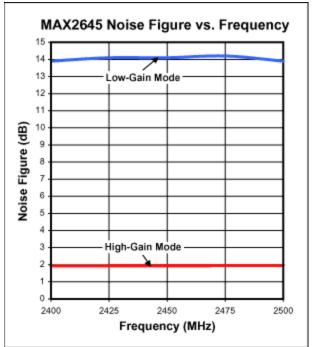


Figure 3. MAX2645 Noise figure versus frequency (VCC = 3.0V, R_{BIAS} = 20k Ω).

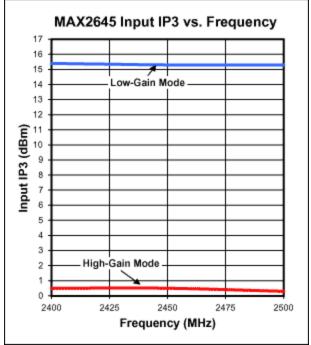


Figure 4. MAX2645 Input IP3 versus frequency ($V_{CC} = 3.0V$, $R_{BIAS} = 20k\Omega$).

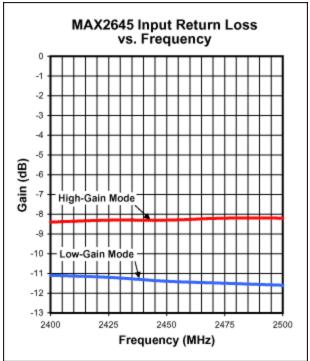


Figure 5. MAX2645 Input Return Loss Versus Frequency ($V_{CC} = 3.0V$, $R_{BIAS} = 20k\Omega$).

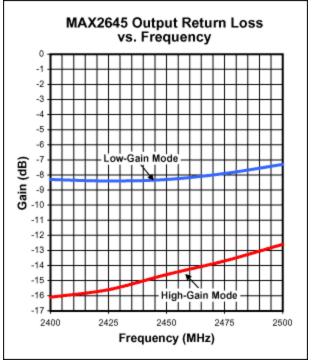


Figure 6. MAX2645 Output return loss ($V_{CC} = 3.0V$, $R_{BIAS} = 20k\Omega$).



3.4GHz to 3.8GHz SiGe Low-Noise Amplifier/PA

Free Samples

More Information

For Technical Support: http://www.maximintegrated.com/support For Samples: http://www.maximintegrated.com/samples Other Questions and Comments: http://www.maximintegrated.com/contact

Application Note 2874: http://www.maximintegrated.com/an2874 APPLICATION NOTE 2874, AN2874, AN 2874, APP2874, Appnote 2874, Appnote 2874 Copyright © by Maxim Integrated Products Additional Legal Notices: http://www.maximintegrated.com/legal